

# Electronic III

---

## **Bipolar Transistor Models**

# Simplified Bipolar Operation

- When the emitter junction is forward biased, it conducts. It consists of majority carriers from emitter (electrons here) and majority carriers from base (holes here).
- Since emitter is much more heavily doped than base, injected electrons from emitter are many more.
- Assuming collector voltage is high (collector-base is reversed biased) no holes from the base will go to the collector.
- However electrons that travel from the emitter to the base, where they are now minority carriers diffuse away from the base-emitter junction due to the minority carriers concentration gradient in base.

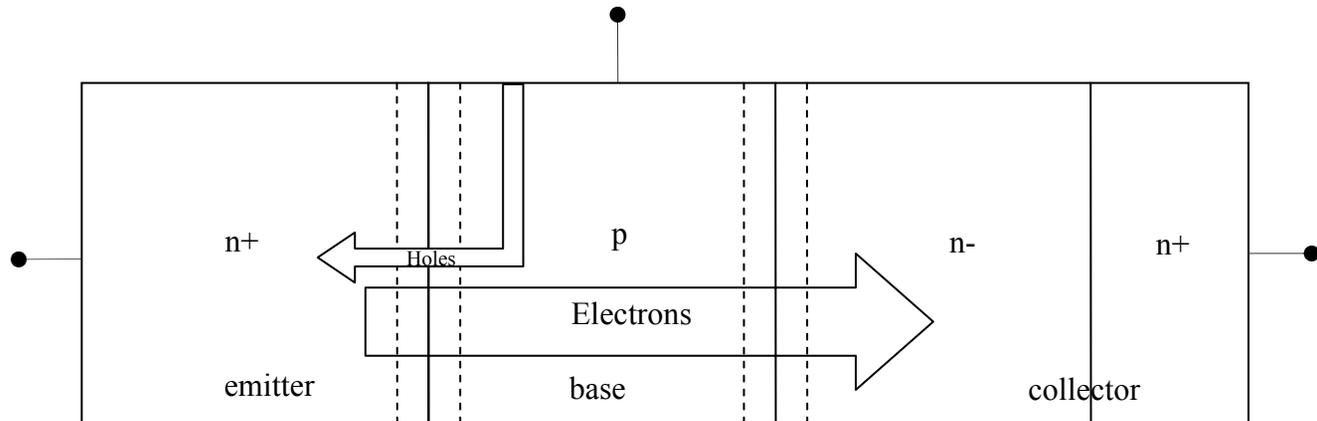


Fig.2.1

# Simplified Bipolar Operation

---

- Any of these electrons that get close to collector-base junction will immediately be “whisked” across the junction due to the large positive voltage on the collector, which attracts electrons.
- In a properly designed **vertical bipolar**, the vertical base width  $W$  (next page figure) is small, so almost all of electrons that diffuse from the emitter to base reach collector-base junction and are swept across junction.
- So the collector current very closely equals the electron current flowing from the emitter to base.
- The much smaller base current very closely equals the current due to the holes that flow from base to emitter.

# Simplified Bipolar Operation


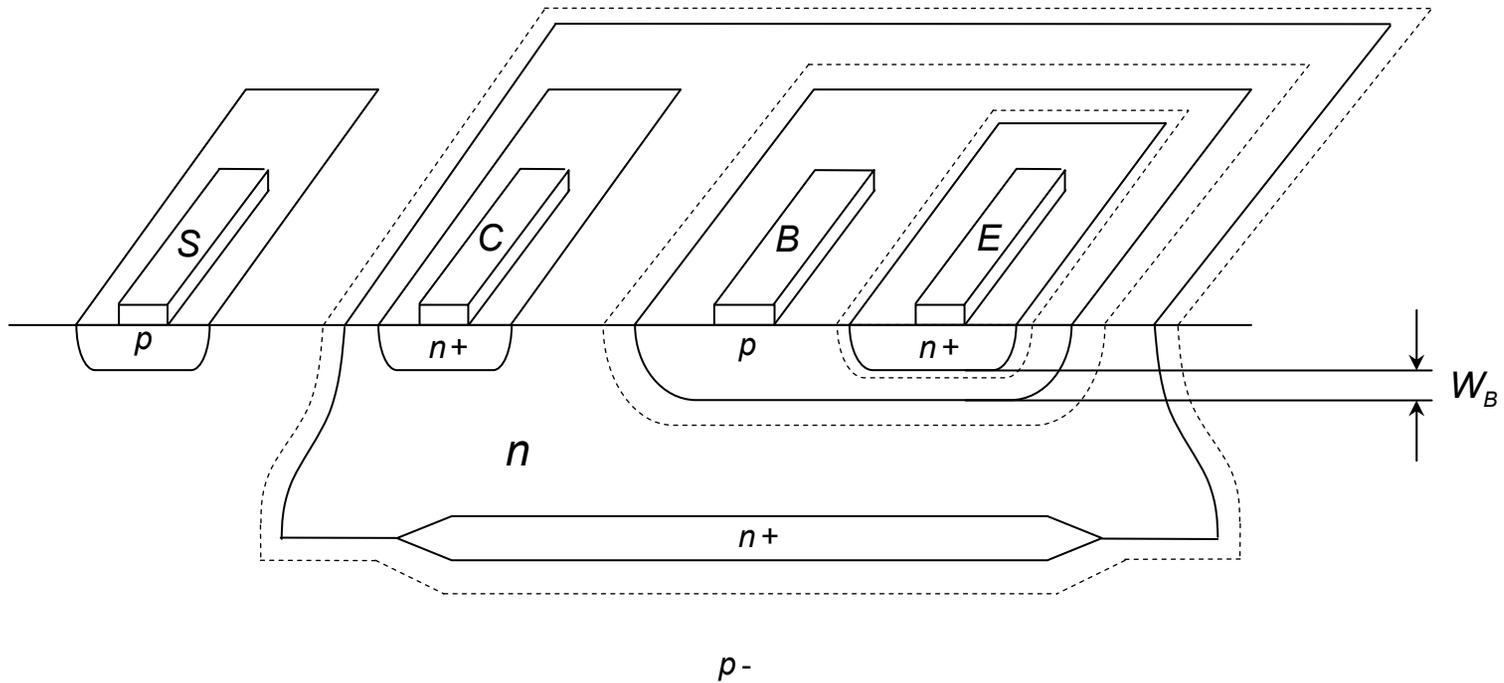


Fig.2.2. The vertical npn bipolar transistor in IC

# The Hybrid- $\pi$ small signal model

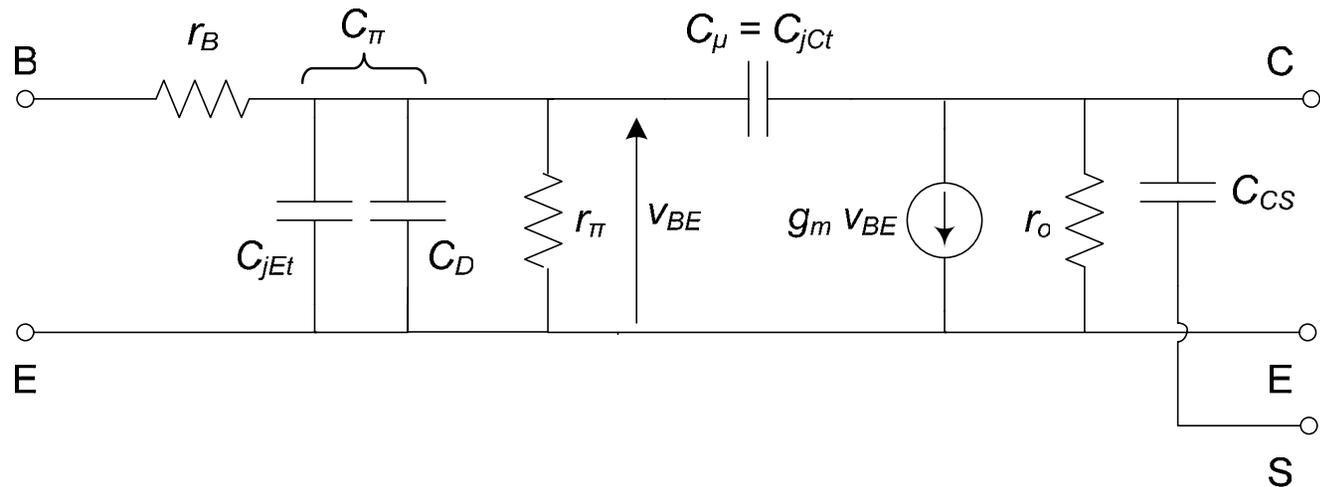

*Fig.2.3. The hybrid- $\pi$  model of bipolar transistor*

# The Hybrid- $\pi$ small signal model

---

$$\left\{ \begin{array}{l} I_C = I_S \exp\left(\frac{v_{BE}}{kq/T}\right) \end{array} \right. \quad (2-1)$$

$$\left\{ \begin{array}{l} I_S = \frac{q A_{EB} D_n n_i^2}{Q_B} \end{array} \right. \quad (2-2)$$

- $Q_B = N_B W_B$  is the integrated charge (per  $\text{cm}^2$  emitter area) in the base.  
 $N_B$  is base doping concentration ( $\text{m}^{-3}$ ).  
 $W_B$  is the base width (m).
- $A_{EB}$  is the EB area ( $\text{m}^2$ ).
- $D_n$  is the diffusion constant for electrons ( $\text{m}^2/\text{sec}$ ). It is related to mobility by Einstein's relation, given by:  $D_n = \mu_n (kT/q)$  .
- $n_i$  is intrinsic silicon electron concentration (at a given temperature) ( $\text{m}^{-3}$ ).  
(@ room temperature  $n_i = 1.5 \times 10^{10} / \text{cm}^3$ )

# The Hybrid- $\pi$ small signal model

- **Tranconductance  $g_m$**

$$g_m = \frac{di_C}{dv_{BE}} = \frac{I_C}{kT/q} \quad (2-3)$$

➤ Directly proportional with  $I_C$ . Doubling the current doubles the Tranconductance.

➤  $\frac{g_m}{I_C} = \frac{q}{kT} = \frac{1}{26\text{mV}}$  @ room temperature larger than the MOST counterpart.

$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{TH}} \Rightarrow \text{for } V_{\text{eff}} = 0.2 \quad \frac{g_m}{I_{DSQ}} = \frac{2}{0.2} = \frac{1}{100\text{mV}}$$

# The Hybrid- $\pi$ small signal model

- **Input Resistance  $r_\pi$**

The ratio of the AC  $V_{BE}$  and the AC  $I_B$  is the AC input resistance. It is called  $r_\pi$  as follows:

$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{dV_{BE}}{dI_C} \frac{dI_C}{dI_B} = \frac{\beta_{AC}}{g_m}$$

Its relationship with  $\beta$  and  $g_m$  is depicted in figure.

$$g_m r_\pi = \beta_{AC} \quad (2-4)$$

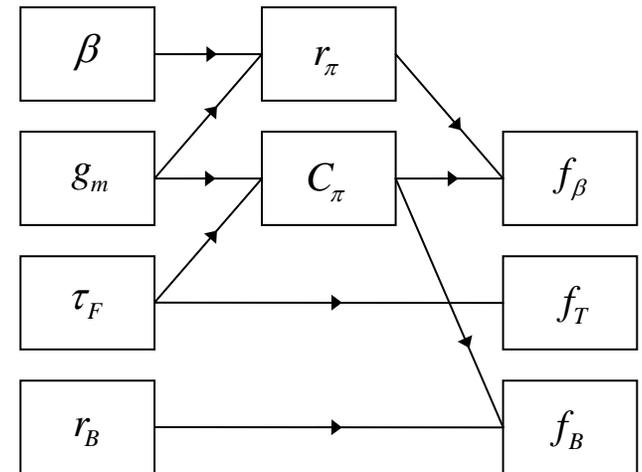


Fig.2.4

# The Hybrid- $\pi$ small signal model

- **Output Resistance  $r_o$**

$r_o$  is the ratio of the AC  $V_{CE}$  to the AC  $I_C$ :  $r_o = \frac{dV_{CE}}{dI_C}$

$$\begin{cases} I_C = I_S \exp\left(\frac{V_{BE}}{kq/T}\right) \\ I_S = \frac{q A_{EB} D_n n_i^2}{Q_B} \end{cases}$$

$$\Delta V_{CE} = \Delta V_{CB} + \Delta V_{BE} = -\Delta V_{BC} \quad \text{Since } V_{BE} = cte$$

$$r_o = \frac{dV_{CE}}{dI_C} = -\frac{dV_{BC}}{dI_C} = -\frac{dV_{BC}}{dQ_B} \left(\frac{dQ_B}{dI_C}\right) \quad (2-5)$$

Increasing  $-V_{BC}$  by  $-\Delta V_{BC}$  increases the width of the depletion layer as shown in next figure. The depletion layer charge increases by  $\Delta Q_B$ .

So less  $Q_B$  is left (the base charge is decreased by the same amount  $\Delta Q_B$ ).

# The Hybrid- $\pi$ small signal model

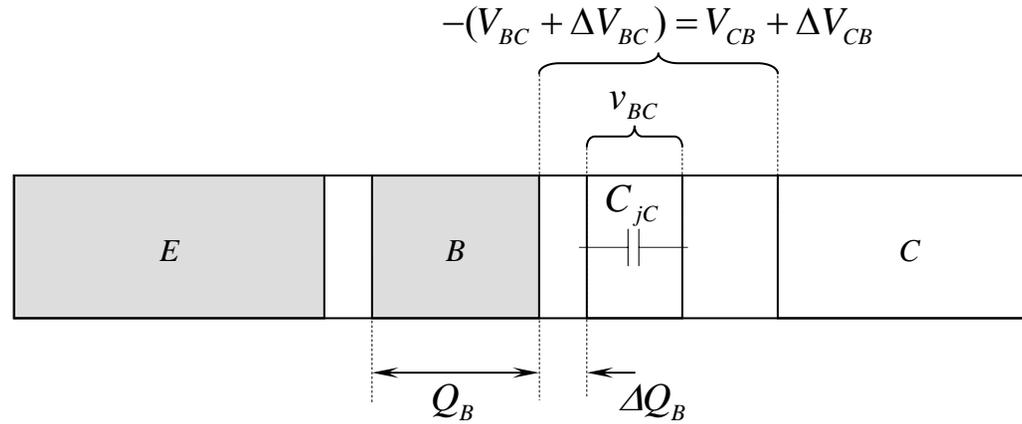


Fig.2.5. Relation between  $\Delta Q_B$  and  $\Delta V_{BC}$  through  $C_{jC}$

Also the variation of the depletion layer charge  $\Delta Q_B$  is linked to the depletion capacitance  $C_{jC}$  (in F/cm<sup>2</sup>) as:

$$q \frac{\Delta Q_B}{\Delta I_C} = C_{jC} \Rightarrow \frac{-dV_{BC}}{-dQ_B} = \frac{q}{C_{jC}}$$

The second term in  $r_o = -\frac{dv_{BC}}{dQ_B} \left( \frac{dQ_B}{dI_C} \right) \dots (2-5)$  is derived from:

$$I_C = \frac{q A_{EB} D_n n_i^2}{Q_B} \exp(V_{EB}/V_T) \Rightarrow \frac{dI_C}{dQ_B} = -\frac{q A_{EB} D_n n_i^2}{Q_B^2} \exp(V_{EB}/V_T) = -\frac{I_C}{Q_B} \quad (2-7)$$

# The Hybrid- $\pi$ small signal model

$$\Rightarrow r_o = \frac{dV_{CE}}{dI_C} = \left(-\frac{dV_{BC}}{dQ_B}\right)\left(\frac{dQ_B}{dI_C}\right) = \left(-\frac{q}{C_{jC}}\right)\left(-\frac{Q_B}{I_C}\right) = \frac{q}{C_{jC}} \frac{Q_B}{I_C}$$

Defining Early voltage as:

$$r_o = \frac{V_A}{I_C} \Rightarrow V_A = \frac{q}{C_{jC}} \frac{Q_B}{I_C} = \frac{q}{C_{jCt}} \frac{A_{BC} Q_B}{I_C} \quad (2-8)$$

$$C_{jCt} = A_{BC} C_{jC}$$

$A_{BC}$  is the total base-collector area.

$C_{jCt}$  is the total base-collector junction capacitance.

Represented by  $C_{\mu}$  in the hybrid- $\pi$  model

# The Hybrid- $\pi$ small signal model

---

- **Small-Signal Voltage Gain  $A_v$**

$$A_v = g_m r_o$$

$$g_m = \frac{I_C}{V_T}, \quad r_o = \frac{V_A}{I_C} \Rightarrow A_v = \frac{V_A}{V_T} = \frac{V_A}{kT/q} \quad (2-9)$$

For  $V_A = 50 \text{ V} \Rightarrow A_v \approx 2000 \text{ V/V}$  or 66 dB

In comparison with BJT gain of MOST stage:

$$A_v = \frac{V_E L}{1/2 V_{eff}} = \frac{1/(2\lambda)}{V_{eff}}$$

# The Hybrid- $\pi$ small signal model

- **Capacitances**

$$C_{\pi} = C_{be} = C_j + C_D$$

Where  $C_j$  is the depletion capacitance of the base-emitter junction. For forward biased junction:

$$C_{jEt} = \frac{A_E C_{jE0}}{\left(1 - \frac{V_{BE}}{\phi_{jE0}}\right)^{m_{jE}}}, \quad m_{jE} = 1/3 \quad (2-10)$$

$$C_{jEt} \approx 2 A_E C_{je0} \quad (2-11)$$

- ***Diffusion Capacitance  $C_D$***

A variation in base-emitter voltage  $\Delta V_{BE}$  causes a variation in injected charge  $\Delta Q_F$ .

$Q_F$ , the dynamic charge is not same as  $Q_B$ .  $Q_F$ , the total integrated charge in the base depends on the forward bias  $V_{BE}$ , where  $Q_B$  is the charge that is physically present in the base. They don't have same dimension either.  $Q_B$ , number of carrier per  $\text{cm}^2$ ,  $Q_F$ , total charge in coulombs.

# The Hybrid- $\pi$ small signal model

This is the charge of minority carriers in base (electrons in npn). This variation causes a variation in majority carriers charge in collector (as explained in BJT operation).

$\Delta Q_F / \Delta v_{BE}$  has the dimension of capacitance and is called the diffusion capacitance.

$$C_D = \frac{dQ_F}{dV_{BE}} = \frac{dQ_F}{dI_C} \frac{dI_C}{dV_{BE}} = \tau_F g_m \quad (2-12)$$

## ➤ **Base Transit Time $\tau_F$**

We can write the current in BJT as follows:

- The more injected minority charge into base, the more current to collector.
- The faster injected charge reach collector (smaller  $\tau_F$ ), the higher collector current is.

As it will be seen:  $\tau_F = \frac{W_B}{v_{sat}}$ ,  $v_{sat}$  is the saturation velocity.

# The Hybrid- $\pi$ small signal model

- This leads to the physical interpretation that  $\tau_F$  is the average time in which the electrons diffuse through the base from the emitter side to the collector side.

It is a measure of the max. frequency:  $f_{T\max} = \frac{1}{2\pi\tau_F}$  (2-13)

*Note:* because of existing channel length modulation, the MOST has  $V_{\text{sat}}$  and max. frequency:

$$f_{\max} = \frac{1}{2\pi} \frac{v_{\text{sat}}}{L_{\text{eff}}}$$

$$C_D = \tau_F g_m = \frac{W_B^2}{2 D_n} g_m = \frac{W_B^2}{2 \mu_n} \frac{I_C}{kT/q} = \frac{W_B^2}{2 \mu_n} \frac{I_C}{(kT/q)^2} \quad (2-14)$$

So physically  $C_D$  is directly proportional with  $W_B^2$  (width of base region squared) and the collector current,  $\mu_n$  and  $kT/q$  are constant.

# The Hybrid- $\pi$ small signal model

- The diffusion capacitance is much larger than the base-emitter junction capacitance. It increases exponentially with  $V_{BE}$ , whereas  $C_{jEt}$  increases only with the square root of  $V_{BE}$ .

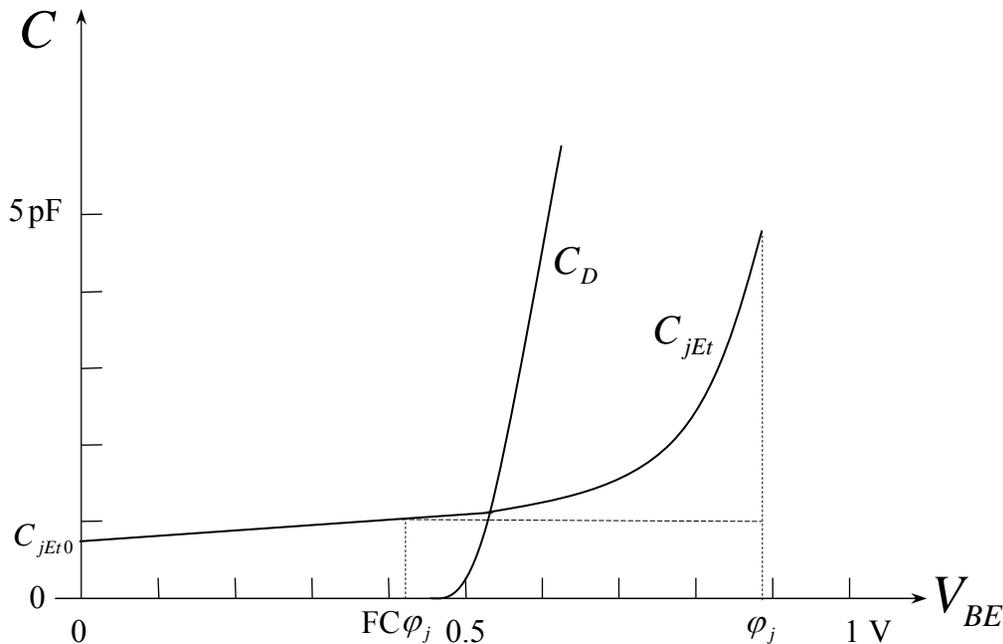


Fig.2.6

# The Hybrid- $\pi$ small signal model

## ➤ **Collector Junction Capacitance $C_\mu$**

$C_\mu$  models the depletion capacitance of the collector-base junction (normally in reverse bias). Since this is a graded junction:

$$C_\mu = C_{jCt} = C_{jCb} = \frac{A_C C_{jC0}}{\left(1 + \frac{V_{CB}}{\phi_{C0}}\right)^{1/3}} \quad (2-15)$$

Where  $A_C$  is the effective area of the collector-base interface.




### Junction Potentials :

$$\varphi_{EB} = \frac{kT}{q} \ln\left(\frac{N_E N_B}{n_i^2}\right) \approx 0.95 \text{ V}$$

$$\varphi_{CB} = \frac{kT}{q} \ln\left(\frac{N_C N_B}{n_i^2}\right) \approx 0.73 \text{ V}$$

$$N_E = 10^{19} / \text{cm}^3, N_B = 2 \times 10^{17} / \text{cm}^3, N_C = 2 \times 10^{15} / \text{cm}^3$$
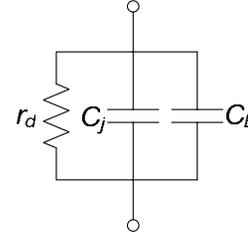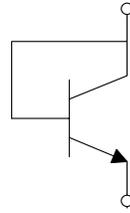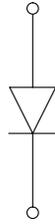
# Small Signal Model for Forward-Biased Diode



$$r_d = \frac{V_T}{I_D}, C_t = C_D + C_j \quad (2-16)$$

$$C_D = \tau_F \frac{I_D}{V_T}, C_j \approx 2C_{j0} \quad (2-17)$$

Where:

$$C_{j0} = \sqrt{\frac{q \epsilon_{si}}{2 \phi_0} \frac{N_D N_A}{N_A + N_D}} \Big|_{N_A \gg N_D} = \sqrt{\frac{q \epsilon_{si} N_D}{2 \phi_0}}$$

$$\text{and } \tau_F = \frac{W_n^2}{2D_n}$$

# The Hybrid- $\pi$ small signal model

## **Base Resistance $r_B$**

The active region of the bipolar transistor is located directly underneath the emitter. The base region is contacted by means of ohmic regions that add series resistance as well as additional capacitance.

For example, a series base resistance  $r_B$  is present between the base contact metal and the active base. It is the most important parasitic series resistance and is included in the hybrid- $\pi$  model.

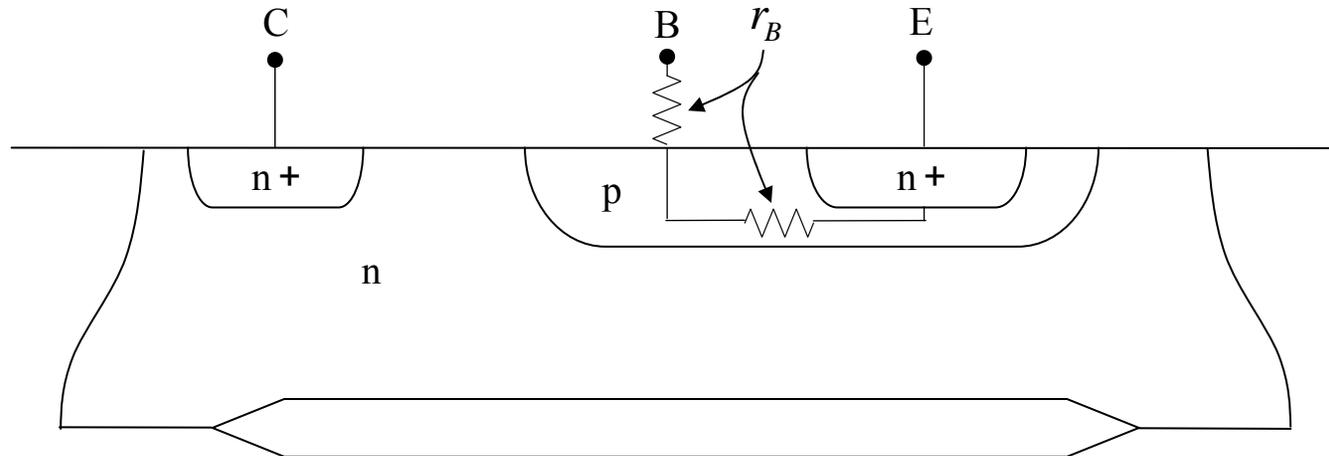


Fig.2.7

## A Simple High-Freq. Model for CE with Current Drive

- In first example we want to realize a *current-gain amplifier*. For this purpose a BJT amplifier, which has a large input source resistance  $R_S$ .
- The AC signal is amplified, then is short circuited by a large cap.  $C_\infty$  to ground, through which we can measure  $i_{Out}$ .

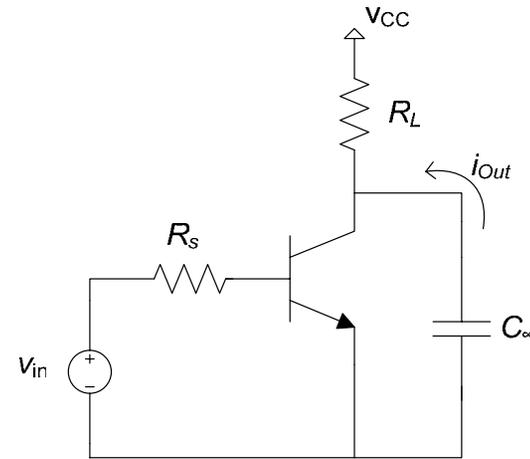


Fig.2.8-a

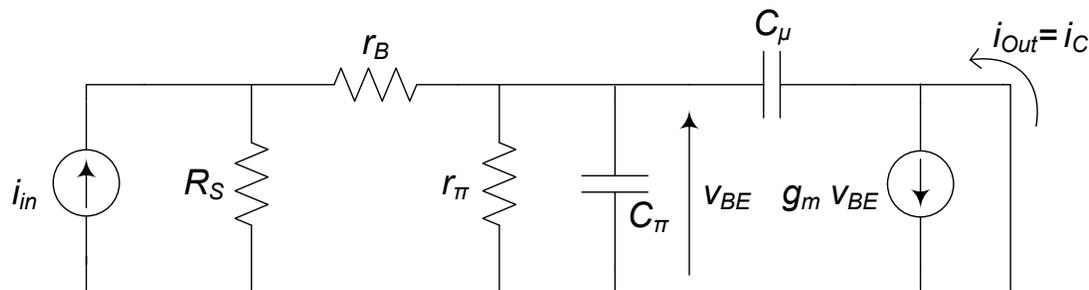


Fig.2.8-b

## A Simple High-Freq. Model for CE with Voltage Drive

- In 2nd example we want to realize a *voltage-to-current amplifier*. For this purpose a BJT amplifier, which has a small input source resistance  $R_S$ .
- The AC signal is amplified, then is short circuited by a large cap.  $C_\infty$  to ground, through which we can measure  $i_{Out}$ .

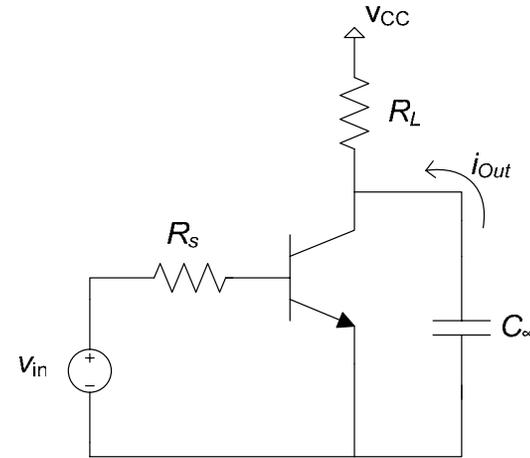


Fig.2.8-a

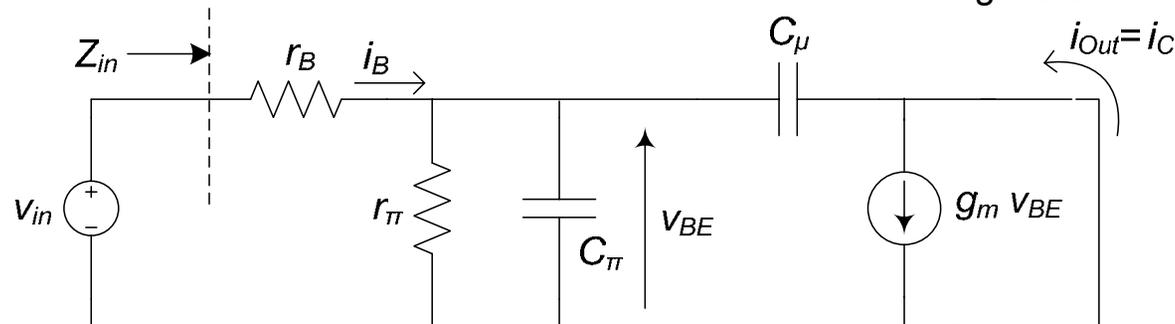


Fig.2.9

## A Simple High-Freq. Model for CE with Current Drive

- Since output is short-circuited  $r_o$  can be left out. A current  $i_C = i_{out}$  flows in the output short circuit.
- $R_S \gg r_\pi + r_B$  therefore the transistor is current driven. Its input current is approximately  $i_{in} = v_{in} / R_S$ .
- $R_S = \infty$ , so from Fig.2.8-b one could say since the input impedance of device is very small compared to  $R_S$  so the input current is almost equal to  $v_{in} / R_S$ .

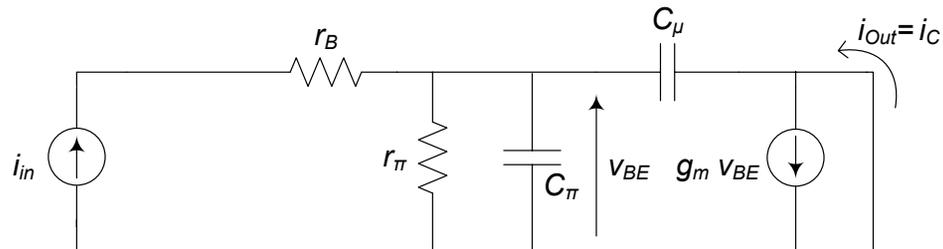


Fig.2.8-c

## A Simple High-Freq. Model for CE with Current Drive

- A common indicator for the speed of a BJT is the frequency at which the transistor current gain drops to unity, when the collector is connected to a small-signal ground:  $f_T$  = Unity-Gain Frequency
- So for  $R_S \gg r_\pi + r_B$  :

$$v_{BE} = i_B \left[ r_\pi + \frac{1}{s(C_\pi + C_\mu)} \right] = i_B \frac{\frac{r_\pi}{s(C_\pi + C_\mu)}}{r_\pi + \frac{1}{s(C_\pi + C_\mu)}} = i_B \frac{r_\pi}{1 + s r_\pi (C_\pi + C_\mu)}$$

This is true for the frequencies near  $f_T$  if:  $f_T \ll g_m / C_\mu$

and  $i_C = g_m v_{BE} \Rightarrow \frac{i_C}{i_B} = \frac{g_m r_\pi}{1 + s r_\pi (C_\pi + C_\mu)}$

$\frac{i_C}{i_B} = \frac{\beta_{AC}}{1 + j f / f_\beta}$  where  $f_\beta = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$  and  $\beta_{AC} = g_m r_\pi$

Note:  $\left| \frac{i_C}{i_B}(\omega) \right| = \frac{g_m r_\pi}{\omega (C_\pi + C_\mu) r_\pi}$  for  $f \gg f_\beta$

for  $\left| \frac{i_C}{i_B}(\omega) \right| = 1 \Rightarrow \omega_T = \frac{g_m}{C_\pi + C_\mu}$  or  $f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)}$  (2-18)

## A Simple High-Freq. Model for CE with Current Drive

$$\beta(j\omega) = A_I = \frac{i_{Out}}{i_{in}} = \frac{\beta_{AC}}{1 + j \frac{f}{f_\beta}} \quad (2-19)$$

$$f_\beta = \frac{f_T}{\beta_{AC}} \quad (2-20)$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \quad \text{Unity - Gain Frequency}$$

$$\Rightarrow f_\beta = f_{-3dB} \quad \text{for current gain } A_I$$

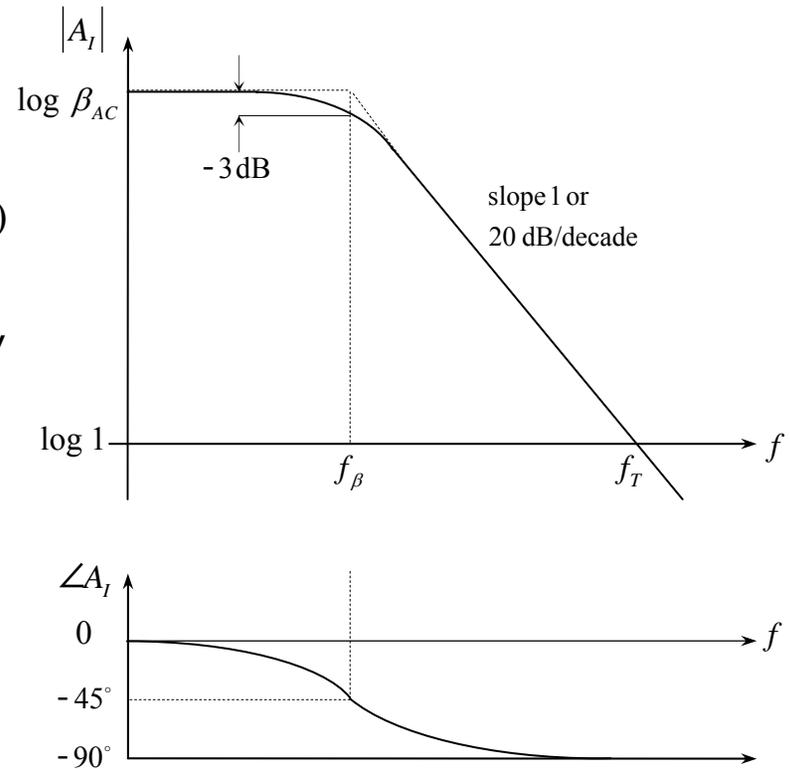


Fig.2.10

## A Simple High-Freq. Model for CE with Current Drive

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} = \frac{g_m}{2\pi(C_D + C_{jEt} + C_\mu)}$$

and  $C_D = g_m \tau_F$

$$\Rightarrow f_T = \frac{g_m}{2\pi(g_m \tau_F + C_{jEt} + C_\mu)}$$

$$= \frac{1}{2\pi \tau_F} \frac{1}{1 + \frac{C_{jEt} + C_\mu}{g_m \tau_F}} \Rightarrow f_T = \frac{1}{2\pi \tau_F} \frac{I_C}{I_C + \frac{I_C (C_{jEt} + C_\mu)}{g_m \tau_F}}$$

$$= \frac{1}{2\pi \tau_F} \frac{I_C}{I_C + (C_{jEt} + C_\mu) \frac{V_T}{\tau_F}}$$

$$\left\{ \begin{array}{l} f_T = \frac{1}{2\pi \tau_F} \frac{I_C}{I_C + I_{CfT}} \end{array} \right. \quad (2-21)$$

$$\left\{ \begin{array}{l} I_{CfT} = (C_{jEt} + C_\mu) \frac{kT/q}{\tau_F} \end{array} \right. \quad (2-22)$$

## A Simple High-Freq. Model for CE with Current Drive

- $f_T$  is reached to its max. value at medium and high currents. The transition current at which this occurs is denoted by  $I_{CfT}$  :

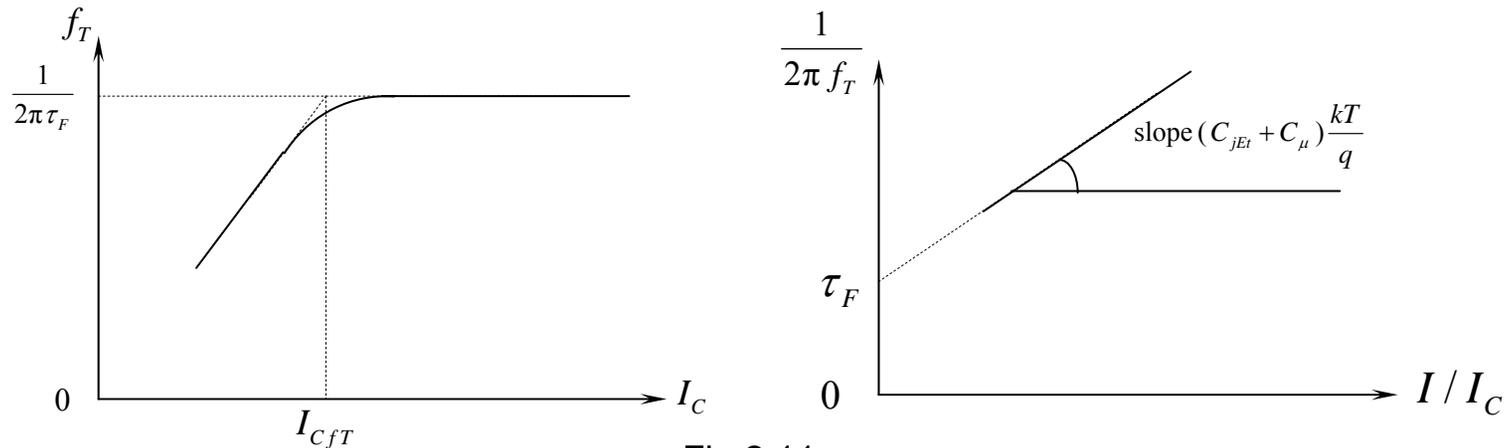


Fig.2.11

- Finally,  $f_T$  is specified for a bipolar transistor with a short-circuited (for AC signal) collector. If an ohmic series resistance  $r_C$  is present, the output can be shorted but there is still some collector resistance that remains.

$$\frac{1}{2\pi f_T} = \tau_F + (C_{jEt} + C_{\mu}) \frac{kT/q}{I_C} + r_C C_{\mu} \quad (2-23)$$

## A Simple High-Freq. Model for CE with Current Drive

### **Example:**

Calculate  $f_\beta$  and  $f_T$  for  $I_C=0.01$  mA, 0.1 mA & 1 mA ?

If  $r_C=30 \Omega$ , what is the  $f_{T\max}$  ?

What is the value of transition current ( $I_{CFT}$ ) ?

$$\beta = 100, \tau_F = 0.25 \text{ ns}, C_{jEt} = 5 \text{ pF}, C_\mu = 1 \text{ pF}$$

### **Solution:**

$$\frac{1}{2\pi f_T} = \tau_F + (C_{jEt} + C_\mu) \frac{kT/q}{I_C}$$

$$I_C = 0.01 \text{ mA} \Rightarrow \frac{1}{2\pi f_T} = 0.25 \times 10^{-9} + (5+1) \times 10^{-12} \times \frac{25 \text{ mV}}{0.01 \text{ mA}} = 15.25 \times 10^{-9}$$

$$f_T = 10.6 \text{ MHz}$$

$$\text{for } I_C = 0.1 \text{ mA} \Rightarrow f_T = 88 \text{ MHz}$$

$$I_C = 1 \text{ mA} \Rightarrow f_T = 393 \text{ MHz}$$

$$f_{T\max} = \frac{1}{2\pi \tau_F} = \frac{1}{2\pi \times 0.25 \times 10^{-9}} = 636 \text{ MHz}$$

## A Simple High-Freq. Model for CE with Current Drive

---

Addition of  $r_C \Rightarrow$


$$\frac{1}{2\pi f_{T\max}} = \tau_F + r_C C_\mu$$

$$\Rightarrow f_{T\max} = \frac{1}{2\pi(\tau_F + r_C C_\mu)} = \frac{1}{2\pi(0.25 \times 10^{-9} + 30 \Omega \times 1 \times 10^{-12})} = 568 \text{ MHz}$$

$$I_{CfT} = (C_{jEt} + C_\mu) \frac{kT/q}{\tau_F} = (5+1) \times 10^{-12} \times \frac{25 \text{ mV}}{0.25 \times 10^{-9}} \cong 0.6 \text{ mA}$$

$$f_T \Big|_{I_C = 0.6 \text{ mA}} = 318 \text{ MHz} = 1/2 f_{T\max}$$
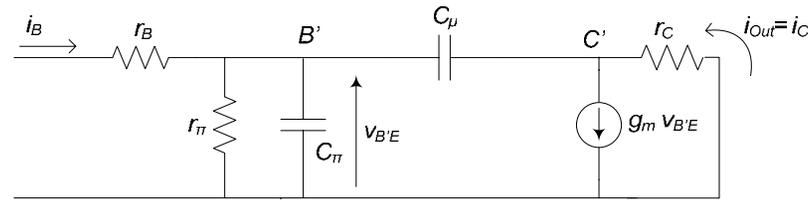
## A Simple High-Freq. Model for CE with Current Drive



An **incorrect** approach:

$$r_B \parallel \left( \frac{1}{s C_\pi} \right) \parallel \left( \frac{1}{s C_\mu + r_C} \right) = r_B \parallel \frac{\frac{1}{s C_\pi} \left( \frac{1}{s C_\mu} + r_C \right)}{\frac{1}{s C_\pi} + \frac{1}{s C_\mu} + r_C} = r_B \parallel \frac{1 + r_C C_\mu s}{s (C_\pi + C_\mu) + s^2 r_C C_\pi C_\mu}$$

$$\frac{v_{B'E}}{i_B} = r_B \parallel \frac{1 + r_C C_\mu s}{s (C_\pi + C_\mu) + s^2 r_C C_\pi C_\mu}$$

$$r_B = 0 \Rightarrow \frac{i_C}{i_B} = \frac{g_m r_\pi (1 + r_C C_\mu s)}{1 + s [r_C C_\mu + r_\pi (C_\mu + C_\pi)] + s^2 r_\pi r_C C_\pi C_\mu}$$

Note: for  $\omega \ll \frac{1}{r_C C_\mu}$  or  $r_C C_\mu s \ll 1$

One can see  $s^2 r_\pi r_C C_\pi C_\mu = (r_C C_\mu s)(r_\pi C_\pi s) \ll (1)(r_C C_\mu s)$

## A Simple High-Freq. Model for CE with Current Drive

So we can ignore the  $s^2$  term compared  
 $s$  term in dominant as well as  
 $r_C C_\mu s$  term in numerator:

$$\text{for } \omega \ll \frac{1}{r_C C_\mu} \Rightarrow \frac{i_C}{i_B}(s) \approx \frac{g_m r_\pi}{1 + s[r_\pi C_\mu + r_\pi (C_\mu + C_\pi)]} \Rightarrow$$

$$f_\beta = \frac{1}{2\pi[(C_\mu + C_\pi)r_\pi + C_\mu r_C]} \quad (2-24)$$

Much more accurate approach:

The voltage across  $C_\mu$ :

$$V_{BC'} \approx V_{be'} - (-g_m r_C V_{be'}) = V_{be'}(1 + g_m r_C)$$

So one can simply replace  $C_\mu$  with  $(1 + g_m r_C)C_\mu$  in previous equation for  $f_T$  (2-18)

$$f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)} \rightarrow f_T = \frac{g_m}{2\pi (C_\pi + C_\mu + g_m r_C C_\mu)}$$

$$\Rightarrow f_T = \frac{1}{2\pi \left( \frac{C_\pi + C_\mu}{g_m} + r_C C_\mu \right)} \quad (2-24)$$

# CE Configuration with Voltage Drive

- **Tranconductance**  $A_G = i_{out} / v_{in}$   
The configuration is the same as below figure but  $R_S$  is much smaller than  $r_{\pi}$ . The small-signal model is shown below (for zero  $R_S$ ).

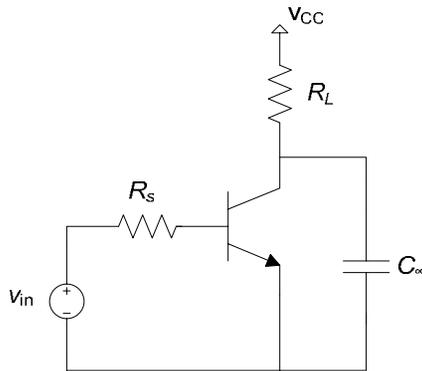


Fig.2.12-a

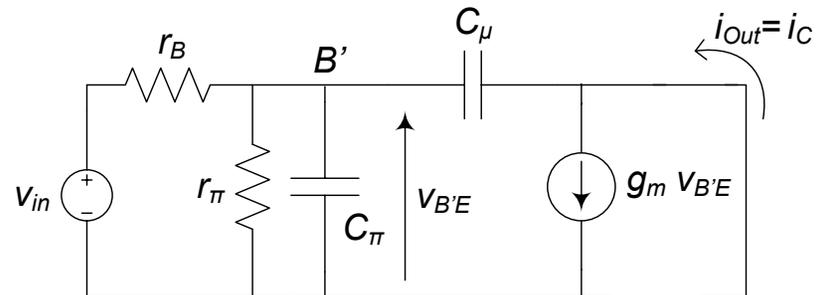


Fig.2.12-b

## Low-Frequency:

Neglect all capacitances.

$$\text{for } r_B \ll r_{\pi} \Rightarrow \frac{i_{Out}}{v_{in}} = g_m$$

# CE Configuration with Voltage Drive

## High-Frequency

$$v'_{BE} = \frac{g_B}{g_B + [g_\pi + s(C_\mu + C_\pi)]} v_{in}$$

$$i_{Out} \approx g_m v'_{BE} \quad \text{neglecting } C_\mu$$

$$\Rightarrow \frac{i_{Out}}{v_{in}} = \frac{i_{Out}}{v'_{BE}} \quad \frac{v'_{BE}}{v_{in}} = g_m \frac{g_B}{g_B + [g_\pi + s(C_\mu + C_\pi)]} = \frac{\frac{g_m g_B}{(g_m + g_B)}}{1 + s \frac{C_\mu + C_\pi}{g_m + g_B}}$$

$$\text{for } g_B \gg g_\pi \quad \text{or} \quad r_B \ll r_\pi \quad \Rightarrow \quad g_B + g_\pi \cong g_B$$

$$\frac{i_{Out}}{v_{in}} \approx \frac{g_m}{1 + s \frac{C_\mu + C_\pi}{g_B}} \Rightarrow A_G = \frac{i_{Out}}{v_{in}} = \frac{g_m}{1 + j f / f_B} \quad (2-25)$$

$$\text{where } f_B = \frac{1}{2\pi r_B (C_\mu + C_\pi)} \quad (2-26)$$

# CE Configuration with Voltage Drive

$\Rightarrow f_B = f_{-3\text{dB}}$  for transconductance current-gain

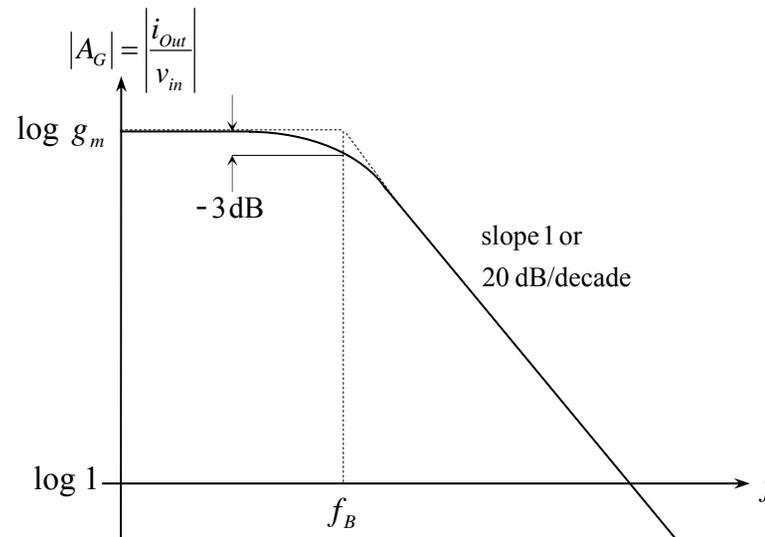


Fig.2.13

Unity-gain frequency for  $A_G$  (Transconductance) is meaningless, i.e. we are not interested to know where  $g_m = 1$  A/V!!

# CE Configuration with Voltage Drive

$$r_B (C_\pi + C_\mu) = r_B (C_D + C_{jEt} + C_\mu) = r_B (C_{jEt} + C_\mu) \left( 1 + \frac{g_m \tau_F}{C_{jEt} + C_\mu} \right)$$

Defining:  $\tau_B = r_B (C_{jEt} + C_\mu)$  (2-27)

$$r_B (C_{jEt} + C_\mu) = \tau_B \left( 1 + \frac{g_m \tau_F}{C_{jEt} + C_\mu} \right) \quad (I)$$

Besides:  $1 + \frac{g_m \tau_F}{C_{jEt} + C_\mu} = 1 + \frac{I_C \tau_F}{\frac{kT}{q} (C_{jEt} + C_\mu)}$

and  $I_{CfT} = (C_{jEt} + C_\mu) \frac{kT/q}{\tau_F}$

$$1 + \frac{g_m \tau_F}{C_{jEt} + C_\mu} = 1 + \frac{I_C}{I_{CfT}} = \frac{I_{CfT} + I_C}{I_C} \quad (II)$$

from (I) & (II) we can rewrite  $f_B$  as follows:

$$f_B = \frac{1}{2\pi r_B (C_\pi + C_\mu)} = \frac{I_{CfT}}{2\pi \tau_B (I_C + I_{CfT})} \quad (2-28)$$


# CE Configuration with Voltage Drive

Note: Can be modified as follows too (by adding collector resistor related time constant):

$$\tau_B = r_B ( C_{jEt} + C_\mu ) + r_C C_\mu$$

$$f_{B\max} = f_B|_{I_C=0} = \frac{1}{2\pi \tau_B} = \frac{1}{2\pi [ r_B ( C_{jEt} + C_\mu ) + r_C C_\mu ]}$$

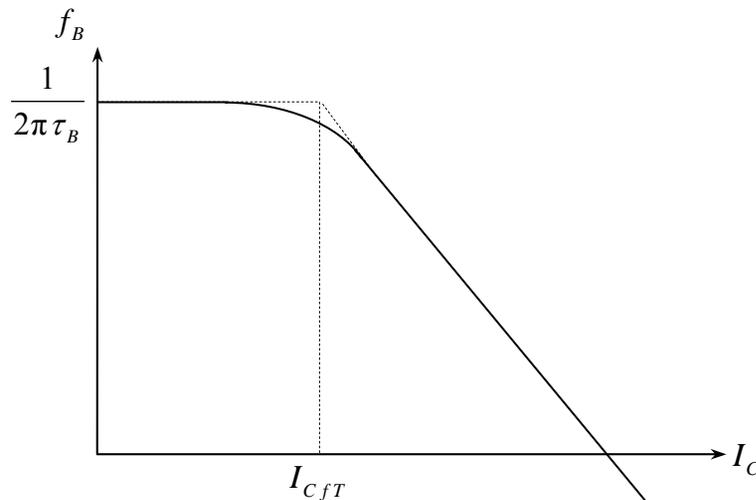from  $f_B = \frac{I_C f_T}{2\pi \tau_B ( I_C + I_{CfT} )}$  plot of  $f_B$  vs.  $I_C$  is as follows:



Decreasing  $I_C$  results increasing of corner frequency of  $f_B$  ( Pole of transconductance) but reduces the value of  $g_m = I_C / V_T$ .

Fig.2.14

# CE Configuration with Voltage Drive

$$\frac{f_B}{f_\beta} = \frac{\frac{1}{2\pi r_B (C_\pi + C_\mu)}}{\frac{1}{2\pi r_\pi (C_\pi + C_\mu)}} = \frac{r_\pi}{r_B} \quad \text{so } f_B > f_\beta \text{ if } r_\pi > r_B$$

So voltage drive BW is larger than current drive BW for  $r_\pi > r_B$ , which is almost always the case; i.e. always  $r_\pi > r_B$

So  $f_B > f_T$  if  $r_B g_m < 1$  or  $r_B < 1/g_m$

$r_B$  could be smaller than  $1/g_m$  for small  $g_m$  (or small  $I_C$ ) values.

Definition: for  $I_C = I_{CTB} = \frac{kT/q}{r_B}$  we have  $f_T = f_B$  because  $r_B = 1/g_m$ .

The max. value of  $f_B$  is reached for current smaller than  $I_{CfT}$ .

$$\text{for } I_C \rightarrow 0 \quad f_{B\max} = \frac{1}{2\pi \tau_B} = \frac{1}{2\pi [r_B (C_{jEt} + C_\mu) + r_C C_\mu]}$$

# CE Configuration with Voltage Drive

---

- This maximum depends only the base resistance and both collector and emitter junction capacitances, and as can be noted it is independent of the base transit time  $\tau_F$ !
- In general, it can be verified that only  $r_B$  limits the high frequency performance of bipolar junction transistor. For  $r_B=0$  infinite BW can be achieved!!!

# CE Configuration with Voltage Drive

## Example:

Calculate  $f_T$ ,  $f_B$ ,  $I_{CTB}$  for  $I_C = 0.01 \text{ mA}$ ,  $0.1 \text{ mA}$ ,  $1 \text{ mA}$  ?

$f_{T\max}$  if  $r_C = 30 \text{ } \Omega$  ?

$\beta = 100$ ,  $\tau_F = 0.25 \text{ ns}$ ,  $C_{jEt} + C_{jCt} = 6 \text{ pF}$ ,  $r_B = 100 \text{ } \Omega$

from previous example:  $f_T = 10 \text{ MHz}$ ,  $88 \text{ MHz}$ ,  $393 \text{ MHz}$  respectively for  $I_C = 0.01 \text{ mA}$ ,  $0.1 \text{ mA}$ ,  $1 \text{ mA}$  .

$$\tau_B = r_B ( C_{jEt} + C_{\mu} ) + r_C \quad C_{\mu} = 100 ( 6 \times 10^{-12} ) + 30 \times 1 \times 10^{-12} = 630 \times 10^{-12} \text{ sec}$$

$$\Rightarrow f_B = \frac{1}{2\pi} \frac{I_{CfT}}{\tau_B I_C + I_{CfT}}$$

$f_B = 248 \text{ MHz}$ ,  $216 \text{ MHz}$ ,  $95 \text{ MHz}$  respectively for  $I_C = 0.01 \text{ mA}$ ,  $0.1 \text{ mA}$ ,  $1 \text{ mA}$  .

$$f_{B\max} = \frac{1}{2\pi \tau_B} = 252.6 \text{ MHz}$$

# CE Configuration with Voltage Drive

---

$$I_C = I_{C f_T} = 0.6 \text{ mA} \Rightarrow f_B = \frac{0.6}{1.2} \frac{1}{2\pi \times 630 \times 10^{-12}} = 126.3 \text{ MHz}$$

The frequency that the  $f_B$  reduce to one half of its DC value

$$I_{CTB} = \frac{kT/q}{r_B} = \frac{25 \text{ mV}}{100} = 0.25 \text{ mA}$$

The current  $I_C$  that the  $f_B = f_T$

$$f_B( I_C = 0.25 \text{ mA} ) = \frac{0.6 \text{ mA}}{0.25 \text{ mA} + 0.6 \text{ mA}} \frac{1}{2\pi \times 630 \times 10^{-12}} \approx 177 \text{ MHz}$$

# Conclusion

- $f_{\beta}$ ,  $f_T$  and  $f_B$  are the most important “frequency” parameters of a bipolar junction transistor (BJT). They all depend on the parameters shown in Fig.2.6:

i.e.  $\beta$ ,  $g_m$ ,  $\tau_F$ ,  $r_B$  and Junction capacitances  $C_{jE1}$ ,  $C_{\mu}$  .

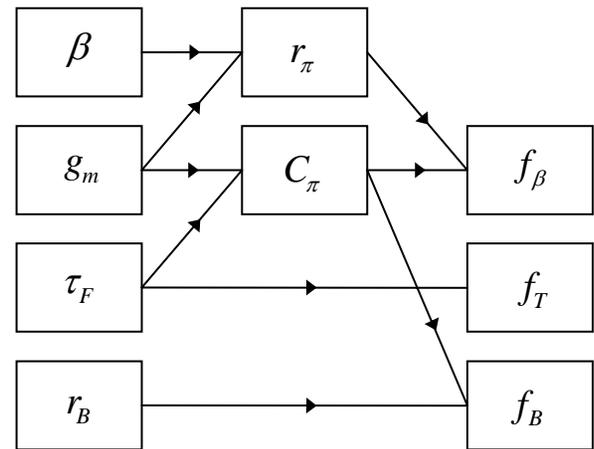


Fig.2.4

$\beta$  and  $\tau_F$  are determined by technology.

$g_m$  can be varied by varying the current  $I_C$ .

$r_B$  can be varied only by taking different (larger) layouts.

# CC and CB Configurations

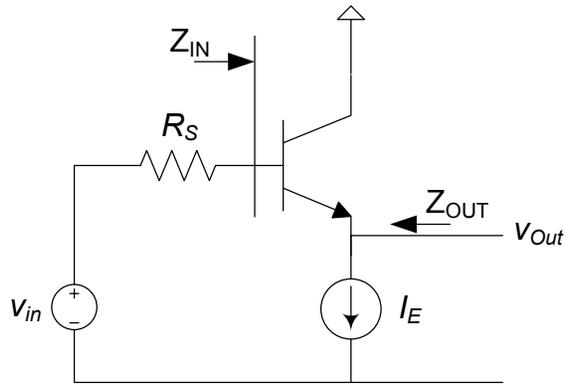


Fig.2.15-a

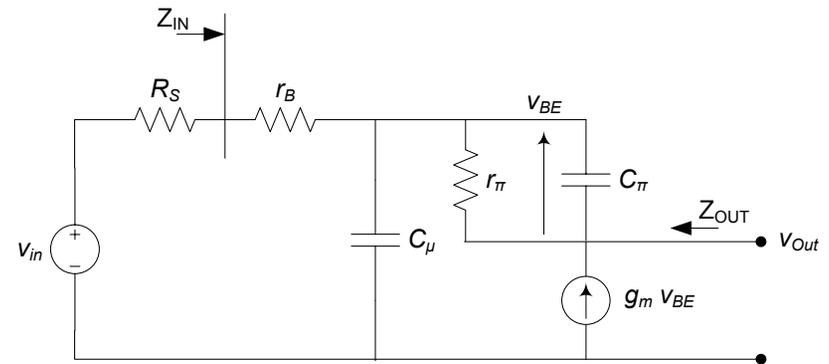


Fig.2.15-b

CC: two bias sources:  $\left\{ \begin{array}{l} 1- \text{ bias voltage at base} \\ 2- \text{ emitter current source} \end{array} \right.$

## **low-frequency**

- $I_E$  with  $1/\beta$  margin error is equal to  $I_C$ . Having a fixed  $I_C$  requires a constant  $V_{BE}$ , so only a DC shift from base to emitter and  $v_{Out} = v_{in}$  and  $Z_{IN} = \infty$ .

# CC and CB Configurations

---

Impedance is converted from high to low :

$$R_{OutLF} = \frac{R_S + r_B + r_\pi}{1 + \beta_{AC}} \quad (2-29)$$

for  $\beta_{AC} \gg 1$  we have:

$$R_{OUTLF} \approx \frac{1}{g_m} + \frac{R_S + r_B}{\beta_{AC}}$$

Note: For MOST  $R_{OUTLF} = \frac{1}{g_m + g_{mb} + g_o} \approx \frac{1}{g_m}$

i.e. source follower

# CC and CB Configurations

## High-Frequency

- At high frequencies caps have to be taken into accounts:

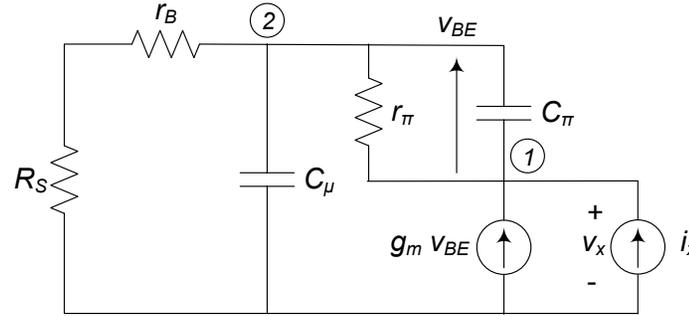


Fig.2.16

$$(1) \quad i_x + g_m v_{BE} + (g_\pi + s C_\pi) v_{BE} = 0$$

$$(2) \quad (g_\pi + s C_\pi) v_{BE} + (g + s C_\mu) (v_{BE} + v_x) = 0 \quad \text{where} \quad g = \frac{1}{r_B + R_S}$$

$$(2) \rightarrow v_{BE} [g_\pi + g + s (C_\mu + C_\pi)] = -v_x (s C_\mu + g)$$

$$\Rightarrow v_{BE} = \frac{-(s C_\mu + g)}{g_\pi + g + s (C_\pi + C_\mu)} v_x \rightarrow \text{into (1)}$$

# CC and CB Configurations

$$\Rightarrow i_x = -v_{BE} (g_m + g_\pi + s C_\pi) = -\frac{(g_m + g_\pi + s C_\pi)(s C_\mu + g)}{g_\pi + g + s(C_\mu + C_\pi)} v_x$$

$$\Rightarrow Z_{OUT} = \frac{v_x}{i_x} = -\frac{g_\pi + g + s(C_\mu + C_\pi)}{(g_\pi + g_m + s C_\pi)(g + s C_\mu)}$$

$$= -\frac{g_\pi + g}{(g_m + g_\pi)g} \frac{1 + s \frac{C_\pi + C_\mu}{g_\pi + g}}{\left(1 + s \frac{C_\pi}{g_m + g_\pi}\right) \left(1 + \frac{C_\mu}{g}\right)}$$

$$= \frac{\left(\frac{1}{r_\pi} + \frac{1}{R_S + r_B}\right)}{\left(g_m + \frac{1}{r_\pi}\right) \left(\frac{1}{R_S + r_B}\right)} \frac{1 + j f / f_Z}{(1 + j f / f_{p1})(1 + j f / f_{p2})}$$

$$f_Z = -\frac{1}{2\pi (C_\pi + C_\mu) [r_\pi \parallel (r_B + R_S)]} \text{ for } R_S = 0 \text{ \& } r_B \ll r_\pi \text{ } f_Z \approx f_B$$

# CC and CB Configurations

$$f_{P1} = -\frac{g_m + g_\pi}{2\pi C_\pi} \approx -\frac{g_m}{2\pi C_\pi} \approx -f_T$$

$$f_{P2} = -\frac{g}{2\pi C_\mu} = -\frac{1}{2\pi (R_S + r_B) C_\mu} \Rightarrow \text{Very high frequency, that can be ignored.}$$

$$\frac{\frac{1}{r_\pi} + \frac{1}{R_S + r_B}}{\left(g_m + \frac{1}{r_\pi}\right) \left(\frac{1}{R_S + r_B}\right)} = \frac{R_S + r_B + r_\pi}{1 + \beta} \approx \frac{1}{g_m} + \frac{R_S + r_B}{\beta} = R_{OUT\ LF}$$

So Provided  $g_m (R_S + r_B) C_\mu \ll C_\pi$  i.e.  $f_{p1} \ll f_{p2}$  :

$$Z_{OUT} = R_{OUT\ LF} \frac{1 + j f/f_B}{1 + i f/f_T} \left\{ \begin{array}{l} f_B = \frac{1}{2\pi r_B (C_\pi + C_\mu)} = \frac{1}{2\pi \tau_B} \frac{I_{CfT}}{I_C + I_{CfT}} \\ \tau_B = r_B (C_{jEt} + C_\mu) + r_C C_\mu \\ f_T = \frac{1}{2\pi \tau_F} \frac{I_C}{I_C + I_{CfT}} \quad (2-30) \\ I_{CfT} = (C_{jEt} + C_\mu) \frac{kT/q}{\tau_F}, \quad \frac{1}{2\pi f_T} = \tau_F + (C_{jEt} + C_\mu) \frac{kT/q}{I_C} + r_C C_\mu \end{array} \right.$$

# CC and CB Configurations

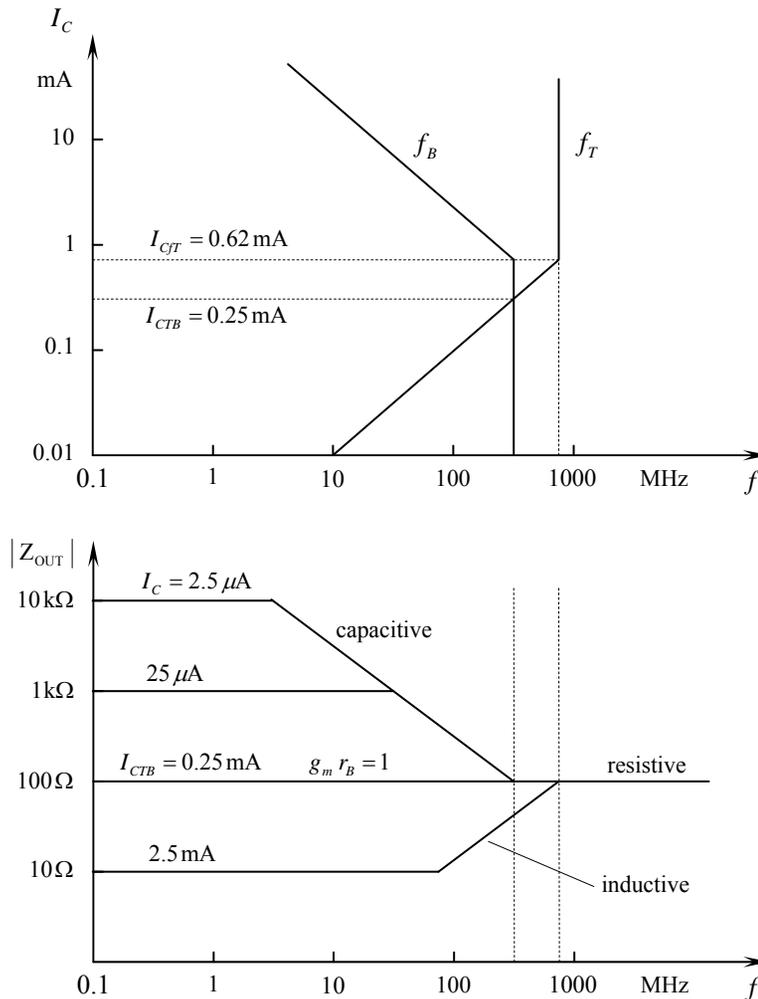


Fig.2.17. Position of pole and zero & bode diagram of  $Z_{OUT}$  of emitter follower for  $\beta = 100$ ,  $r_B = 100 \Omega$ ,  $\tau_F = 0.25 \text{ ns}$ ,  $C_{jEt} + C_\mu = 6 \text{ pF}$ .

# CC and CB Configurations

$$Z_{\text{OUT}}(jf) = R_{\text{OUT LF}} \frac{1 + jf/f_B}{1 + jf/f_T}$$

$$\text{neglecting } \frac{R_S + r_B}{\beta} \Rightarrow |Z_{\text{OUT}}(jf)|_{f \rightarrow \infty} = \left( \frac{1}{g_m} \right) \times \frac{f_T}{f_B}$$

$$= \left( \frac{1}{g_m} \right) \frac{\frac{g_m}{2\pi(C_\pi + C_\mu)}}{1} \Rightarrow \frac{2\pi r_B (C_\pi + C_\mu)}{2\pi r_B (C_\pi + C_\mu)}$$

$$|Z_{\text{OUT}}(jf)|_{f \rightarrow \infty} = \left( \frac{1}{g_m} \right) (g_m r_B) = r_B$$

- So for every  $I_C$  the output impedance of the emitter follower at very high frequency is equal to  $r_B$ .
- So note that at  $I_{\text{CBT}}$  we have  $r_B = \frac{1}{g_m} \Big|_{I_C = I_{\text{CTB}}} = \frac{V_T}{I_{\text{CTB}}}$ .

# CC and CB Configurations

---

- In previous figure, the asymptotic values of  $f_B$  and  $f_T$  are plotted versus  $I_C$ . This plot gives the positions of the zero and the pole with  $I_C$  as so is called pole-zero position plot.
- @  $I_{CTB}$ ,  $g_m r_B = 1$  :  $f_T = f_B$  so a pure resistance results, i.e.  $r_B$ .
- At lower  $I_C$ ,  $f_T$  (pole)  $<$   $f_B$  (zero) so the output impedance rolls off vs. frequency (*capacitive*).
- At higher  $I_C$ ,  $f_B < f_T$ . so there is a region in which output impedance increases with frequency. This region is called an *inductive region*.
- This inductance could cause instability if combined with parasitic cap. at output terminal, so it is safer to reduce the biasing current.

# CC and CB Configurations

---

- Note previous results obtained for

$$R_S \ll r_B \ll r_\pi \Rightarrow f_Z \approx f_B$$

- However, for (perhaps more practical case)

$$r_B \ll r_\pi \ll R_S \Rightarrow f_Z \approx f_\beta = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

moves to a lower frequency

$$f_{p1} = f_T \text{ unchanged; and } f_{p2} = \frac{C_\mu}{g} \approx R_S C_\mu$$

moves to a higher frequency

# CB Configurations

---

- The input impedance of CB is exactly the same as the output impedance of the Emitter-Follower. So the same pole-zero position plot can be used for CB input impedance.
- Particularly the previous assumption for the source impedance could be more practical:  $R_S \ll r_B \ll r_\pi \Rightarrow f_Z \approx f_B$

# Comparison between MOSTs and Bipolar transistors

## ➤ Maximum Frequency of Operation:

$f_T$  is assumed as the parameter (unity-gain of amplifier can be discussed too!).

from bipolar:  $f_{T\max} = \frac{1}{2\pi\tau_F}$  where  $\tau_F = \frac{W_B}{v_{\text{sat}}}$

for MOST, it can be shown that:

$$\tau_F = \frac{L_{\text{eff}}}{v_{\text{sat}}}$$

- $\tau_F$  (transit time) for bipolar is likely to be smaller for a bipolar transistor than for a MOST because the vertical  $W_B$  is easier to make smaller than the lateral  $L_{\text{eff}}$ . [for 0.1  $\mu\text{m}$ , this time constant is about 1 ps  $\Leftrightarrow f_T \approx 160$  GHz]

# Comparison between MOSTs and Bipolar transistors

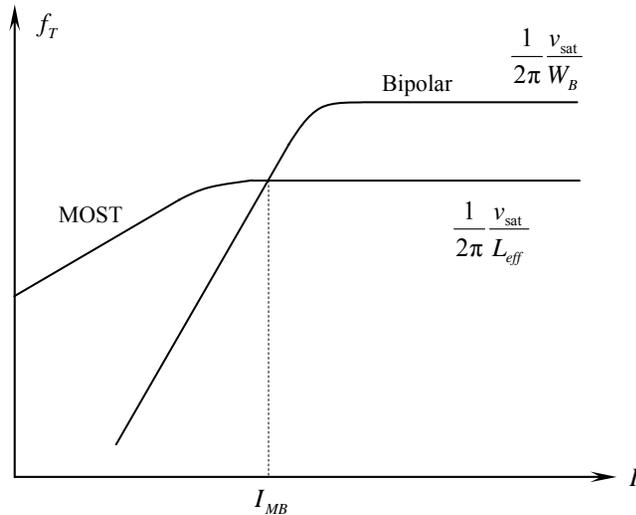


Fig.2.18

- When saturation velocity and so the drain saturation current happens well before pinch-off!

$$I_D = v_{sat} Q_d = v_{sat} W C_{ox} (V_{GS} - V_{TH}) \quad (2-31)$$

$$\Rightarrow g_{m,sat} = W C_{ox} v_{sat} \quad (2-32)$$

$$f_{T\max} = \frac{1}{2\pi} \frac{g_{m,sat}}{C_{GS}} \approx \frac{1}{2\pi} \frac{W C_{ox} v_{sat}}{W L_{eff} C_{ox}} = \frac{1}{2\pi} \frac{v_{sat}}{L_{eff}} \quad (2-33)$$

## Comparison between MOSTs and Bipolar transistors

- In long-channel since the quadratic relations already exist:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \Rightarrow g_m = \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})$$

$$\Rightarrow f_{Tmax} = \frac{1}{2\pi} \frac{g_m}{C_{GS}} = \frac{1}{2\pi} \frac{\mu_n C_{ox} W / L_{eff} (V_{GS} - V_{TH})}{W L_{eff} C_{ox}} = \frac{1}{2\pi} \frac{\mu_n}{L_{eff}^2} (V_{GS} - V_{TH}) \quad (2-34)$$

- In short-channel considering short-channel effects (i.e. mobility degradation)

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{(V_{GS} - V_{TH})^2}{1 + \theta(V_{GS} - V_{TH})} \quad \text{where } \theta = \frac{1}{L_{eff} E_C} \quad (2-35)$$

- As shown in the Fig.2.18 increasing  $I_D$  beyond some point makes  $f_T$  saturated. This can be somehow explained by equations 2-32 & 2-35. Increasing  $I_D$  is done by increasing  $(V_{GS} - V_{TH})$ . For very large  $I_D$  and so  $(V_{GS} - V_{TH})$  if  $\theta(V_{GS} - V_{TH}) \gg 1$  then 2-35 becomes:

$$I_D = \frac{1}{2} \frac{\mu_0 C_{ox} W}{\theta L} (V_{GS} - V_{TH}) = \frac{1}{2} \mu_n E_C W C_{ox} (V_{GS} - V_{TH}), \mu_0 = \frac{v_{sat}}{E_C} \quad (2-36)$$

# Comparison between MOSTs and Bipolar transistors

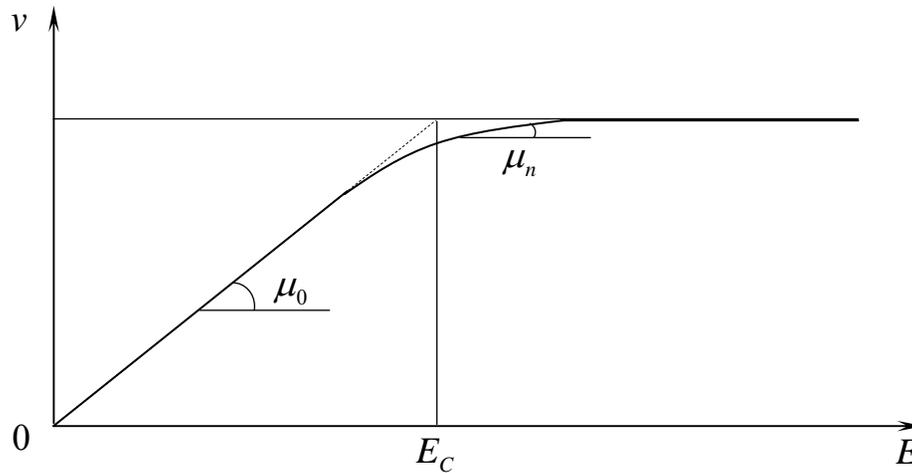


Fig.2.19

# Comparison between MOSTs and Bipolar transistors

## ➤ Tranconductance-Current Ratio:

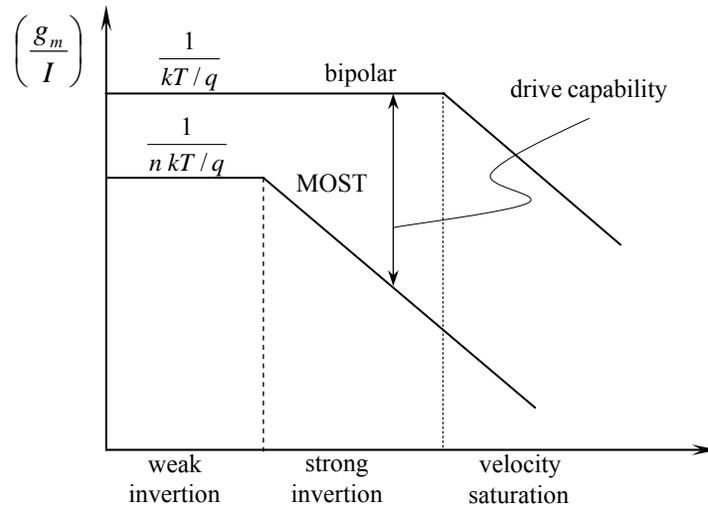


Fig.2.20

- Bipolar offers a better current drive capability. Less input voltage is required to drive a larger output current!