



Multistage Amplifier Frequency Response

Multistage Amplifier Freq. Response

Dominant-pole Approximation:

$$A(s) = \frac{N(s)}{D(s)} = \frac{a_0 + a_1s + a_2s^2 + \dots + a_ms^m}{1 + b_1s + b_2s^2 + \dots + b_ns^n} \quad (7.64)$$

a_0, a_1, \dots, a_m and b_1, b_2, \dots, b_n are constant.

For All-pole system (when there is no dominant zero!) :

$$A(s) = \frac{K}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \dots \left(1 - \frac{s}{p_n}\right)} \quad (7.65)$$

Where K is a constant and p_1, p_2, \dots, p_n are the poles.

Multistage Amplifier Freq. Response

From (7.64) and (7.65) :

$$b_1 = \sum_{i=1}^n \left(-\frac{1}{p_i} \right) \quad (7.66)$$

An important practical case:

$$|p_1| \ll |p_2|, |p_3|, \dots \text{ so that } \left| \frac{1}{p_1} \right| \gg \left| \sum_{i=2}^n \left(-\frac{1}{p_i} \right) \right|$$
$$\Rightarrow b_1 = \left| \frac{1}{p_1} \right| \quad (7.67)$$

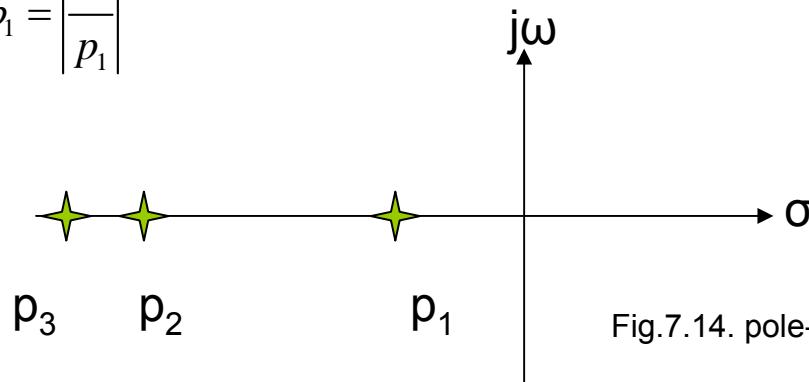


Fig.7.14. pole-plot with dominant pole.

Multistage Amplifier Freq. Response

From (7.65) the gain is:

$$|A(j\omega)| \approx \frac{K}{\sqrt{1 + \left(\frac{\omega}{p_1}\right)^2}}, \omega \leq p_1 \quad (7.69)$$

If a dominant pole exists then:

$$|A(j\omega)| = \frac{K}{\sqrt{\left[1 + \left(\frac{\omega}{p_1}\right)^2\right] \left[1 + \left(\frac{\omega}{p_2}\right)^2\right] \dots \left[1 + \left(\frac{\omega}{p_n}\right)^2\right]}} \quad (7.68)$$

This approximation is quite accurate at least until $\omega = |p_1|$, so:

$$\left. \begin{aligned} \omega_{-3dB} &= |p_1| & (7.70) \\ \omega_{-3dB} &\approx \frac{1}{b_1} & (7.71) \end{aligned} \right\} \rightarrow \text{dominant pole situation!}$$



Zero-Value Time-Constant Analysis

This is an approximate method of analysis that allows an estimate to be made of the dominant-pole freq. (-3dB freq.) of complex circuits.

Zero-Value Time-Constant Analysis

Consider the circuit shown in fig.7.15:

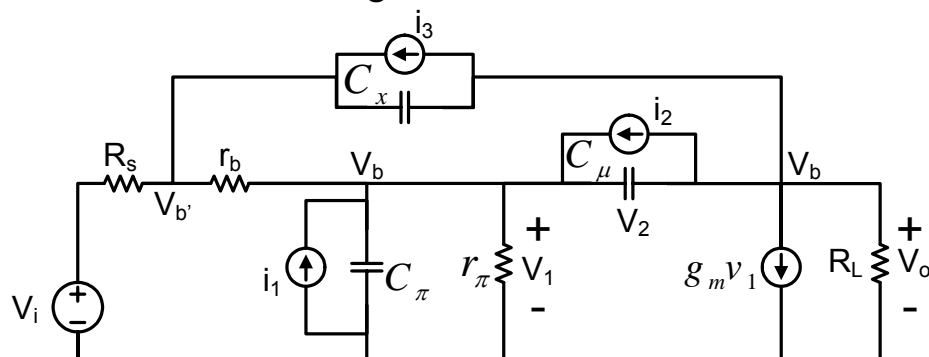


Fig.7.15: A CE circuit with internal Caps.

For analysis, the cap voltages, V_1 , V_2 , and V_3 are chosen as variables. The external input V_i is removed and the circuit excited with three independent current sources i_1 , i_2 and i_3 across the caps:

$$\begin{cases} i_1 = (g_{11} + sC_\pi)v_1 + g_{12}v_2 + g_{13}v_3 \end{cases} \quad (7.72)$$

$$\begin{cases} i_2 = (g_{21})v_1 + (g_{22} + sC_\mu)v_2 + g_{23}v_3 \end{cases} \quad (7.73)$$

$$\begin{cases} i_3 = g_{31}v_1 + g_{32}v_2 + (g_{33} + sC_x) \end{cases} \quad (7.74)$$

Zero-Value Time-Constant Analysis

The g terms are conductions. Note that terms involving s contributed by the caps are associated only with their respective cap voltage and appear only on the diagonal of the system determinant.

$$\Delta(s) = k_3 s^3 + k_2 s^2 + k_1 s + k_0 = k_0 (1 + b_1 s + b_2 s^2 + b_3 s^3) \quad (7.75), (7.76)$$

we showed previously that if there are no dominant zeros, and if there is a dominant pole, then:

$$\omega_{-3dB} \approx \frac{1}{b_1}$$

Zero-Value Time-Constant Analysis

Poles of the transfer function are zeros of determinant Δ :

$$\Delta(s) = k_3 s^3 + k_2 s^2 + k_1 s + k_0 \quad (7.75)$$

from (7.75):

$$\Delta(s) = k_0 (1 + b_1 s + b_2 s^2 + b_3 s^3) \quad (7.76)$$

$$b_1 k_0 = k_1 \Rightarrow b_1 = \frac{k_1}{k_0}$$

This form is like (7.64).

Note that this is a 3rd-order determinant because there are three caps in the circuit.

Zero-Value Time-Constant Analysis

K_0 in (7.75) is the value of $\Delta(s)$ if all caps ($C_x=C_\mu=C_\pi=0$):

\Rightarrow from (7.72), (7.73), (7.74):

$$\left\{ \begin{array}{l} k_0 = \Delta \Big|_{C_\pi=C_\mu=C_x=0} \\ k_0 \triangleq \Delta_0 \end{array} \right\} \quad (7.77)$$

Consider now the term k_1s in (7.75) from (7.72)-(7.74).

It is apparent that s only occurs when associated with a capacitance.

$$\Rightarrow k_1s = h_1sC_\pi + h_2sC_\mu + h_3sC_x \quad (7.78)$$

Where h terms are constants.

Zero-Value Time-Constant Analysis

h_1 can be evaluated by expanding the determinant of (7.72) to (7.74) about the first row:

$$\Delta(s) = (g_{11} + sC_\pi)\Delta_{11} + g_{12}\Delta_{12} + g_{13}\Delta_{13} \quad (7.79)$$

Where Δ_{11} , Δ_{12} and Δ_{13} are cofactors of determinant.

↘ Which includes C_μ and C_x terms! (no C_π)

(7.72) to (7.74) show that C_π only occurs in the first term of (7.79), Δ_{12} has only C_x and Δ_{13} has C_μ . In Δ_{11} both C_x and C_μ exists.

Therefore the coefficient of sC_π in (7.78) is found by evaluating Δ_{11} with $C_\mu=C_x=0$ which eliminates the other capacitive terms in Δ_{11} .

We need to set $C_\mu=C_x=0$. Otherwise the order of coefficient of C_π will be higher than s^1 .

Zero-Value Time-Constant Analysis

The coefficient of sC_π is h_1 in (7.78):

$$h_1 = \Delta_{11} \Big|_{C_\mu = C_x = 0} \quad (7.80)$$

Now we expand the determinant about the second row:

$$\Delta(s) = g_{21}\Delta_{21} + (g_{22} + sC_\mu)\Delta_{22} + g_{23}\Delta_{23} \quad (7.81)$$

C_μ occurs only in 2nd term in (7.81). [Δ_{21} has only C_x and Δ_{23} has only C_π]

Zero-Value Time-Constant Analysis

The coefficient of sC_μ is found by evaluating Δ_{22} when $C_\pi=C_x=0$, which eliminate the other Cap terms in Δ_{22} (which includes both C_π and C_x terms!).

This coefficient of sC_μ is h_2 in (7.78):

$$h_2 = \Delta_{22}|_{C_\pi=C_x=0} \quad (7.82)$$

Similarly by expanding about 3rd-row:

$$h_3 = \Delta_{33}|_{C_\pi=C_\mu=0} \quad (7.83)$$

Zero-Value Time-Constant Analysis

Combining (7.78) with [(7.80),(7.82) and (7.83)] we have:

$$k_1 = \left(\Delta_{11}|_{C_\mu=C_x=0} \times C_\pi \right) + \left(\Delta_{22}|_{C_\pi=C_x=0} \times C_\mu \right) + \left(\Delta_{33}|_{C_\mu=C_\pi=0} \times C_x \right) \quad (7.84)$$

\Rightarrow

$$b_1 = \frac{k_1}{k_0} = \left(\frac{\Delta_{11}|_{C_\mu=C_x=0}}{\Delta_0} \right) \times C_\pi + \left(\frac{\Delta_{22}|_{C_\pi=C_x=0}}{\Delta_0} \right) \times C_\mu + \left(\frac{\Delta_{33}|_{C_\mu=C_\pi=0}}{\Delta_0} \right) \times C_x \quad (7.85)$$

Now consider $i_2=i_3=0$ in fig. 7.15.

Solving Eqns. (7.72)-(7.74) for v_1 gives:

$$v_1 = \frac{\Delta_{11}}{\Delta(s)} i_1 \Rightarrow \frac{v_1}{i_1} = \frac{\Delta_{11}}{\Delta(s)} \quad (7.86)$$

Zero-Value Time-Constant Analysis

This is the driving point impedance at C_π node pair and,

$$\frac{\Delta_{11}|_{C_\mu=C_x=0}}{\Delta_0}$$

Is the driving-point resistance at the node pair when all caps are equal to zero because:

$$\frac{\Delta_{11}|_{C_\mu=C_x=0}}{\Delta_0} = \frac{\Delta_{11}}{\Delta} \Big|_{C_\mu=C_x=C_\pi=0} \quad (7.87)$$

We define:

$$R_{\pi 0} = \frac{\Delta_{11}}{\Delta_0} \Big|_{C_\mu=C_x=0} \quad (7.88)$$

Zero-Value Time-Constant Analysis

Similarly:

$$R_{\mu 0} = \frac{\Delta_{22}|_{C_{\pi}=C_x=0}}{\Delta_0}$$

Is the driving point resistance at the C_{μ} node pair with all capacitors put equal to zero.

therefore from (7.85) we can write:

$$b_1 = R_{\pi 0} C_{\pi} + R_{\mu 0} C_{\mu} + R_{x0} C_x \quad (7.89)$$

The time constant in (7.89) are called “zero-value time constant” because all caps are put equal to zero to perform the calculation.

Zero-Value Time-Constant Analysis

Thus:

$$\omega_{-3dB} \approx \frac{1}{\sum T_o} \quad (7.90)$$

Where $\sum T_o$ is the sum of the Zero-Value time constants.

for circuit of fig.7.15 one can show:

$$b_1 = R_{\pi 0} C_{\pi} + R_{\mu 0} C_{\mu} + R_{x0} C_x \quad (7.89)$$

Where $R_{\pi 0}$ is the driving-point resistance at C_{π} node pair with all capacitors equal to zero.

Zero-Value Time-Constant Analysis

$R_{\mu 0}$ is the driving-point resistance at C_{μ} node pair with all Caps equal to zero, and R_{x0} the same for C_x .

Although derived in terms of a specific example, this result is true in any circuit for which the assumptions made in this analysis are valid! (such as no dominant zero and a dominant pole!)

Zero-Value Time-Constant Analysis (Ex.)

For C_{π} , by inspection:

$$R_{\pi 0} = r_{\pi} \parallel (R_s + r_b) \quad (7.91)$$

For C_{μ} : we apply a test current i at the C_{μ} terminals as shown in fig.7.16.

$$v_1 = R_{\pi 0} i \quad (7.92)$$

$$v_o = -(i + g_m v_1) R_L \quad (7.93)$$

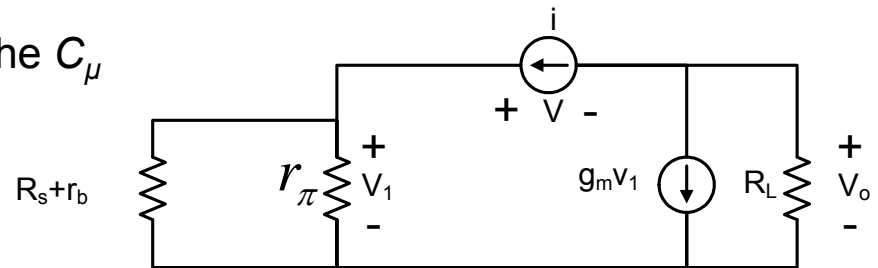


Fig. 7.16

$$(7.92) \text{ into } (7.93): \quad v_o = -(i + g_m R_{\pi 0} i) R_L \quad (7.94)$$

$$R_{\mu 0} = \frac{v}{i} \quad \text{and} \quad R_{\mu 0} = \frac{v_i - v_o}{i} \quad (7.95)$$


(7.92) and (7.94) in (7.95):

$$R_{\mu 0} = R_{\pi 0} + R_L + g_m R_L R_{\pi 0} \quad (7.96)$$

Emitter-Follower (Cont'd)

Why $R_b \ll r_\pi$ results in $R_{x0} \approx R_{\mu0}$?

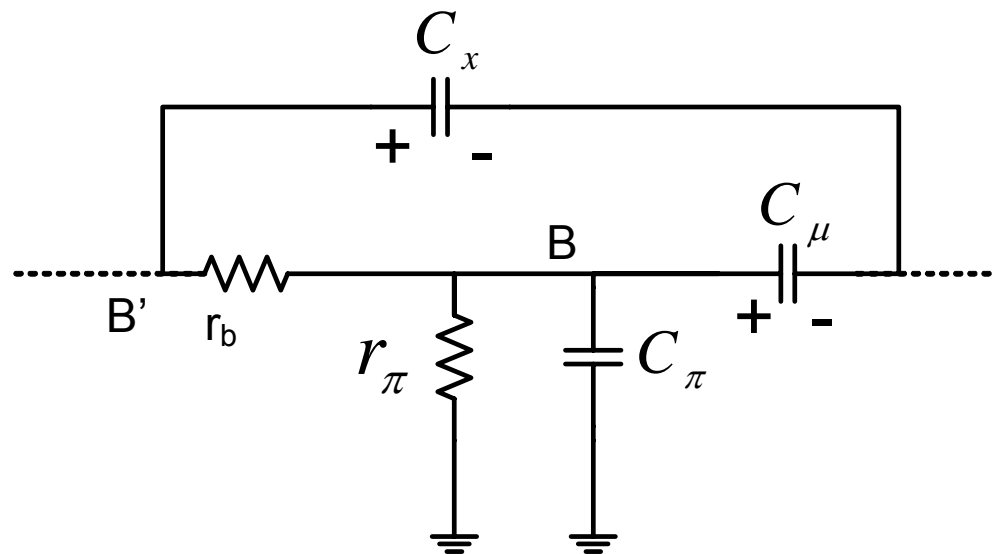The negative plates of C_μ and C_x are tied together. So if we have their positive plates tied too then C_μ will be in parallel with C_x having identical driving-point resistance (i.e. $R_{x0} \approx R_{\mu0}$).



Emitter-Follower (Cont'd)

It is obvious at least in DC that if $R_b \ll r_\pi$ then:

$$\frac{V_B}{V_{B'}} = \frac{r_\pi}{r_\pi + r_b} \bigg|_{r_b \ll r_\pi} \approx 1$$

So the approximation $R_b \ll r_\pi$ leads to $R_{x0} \approx R_{\mu0}$!

Zero-Value Time-Constant Analysis (Ex.)

R_{x0} can be calculated in a similar fashion. It is obvious that

$$R_{x0} \approx R_{\mu0} \quad \text{if} \quad r_b \ll r_\pi$$

C_x can be lumped in with C_μ if r_b is small:

$$\omega_{-3dB} = \frac{1}{R_{\pi0}C_x + R_{\mu0}C_\mu} \quad (7.97)$$

$$\omega_{-3dB} = \frac{1}{R_{\pi0} \left\{ C_\pi + C_\mu \left[(1 + g_m R_L) + \frac{R_L}{R_{\pi0}} \right] \right\}} \quad (7.98)$$

Zero-Value Time-Constant Analysis (Ex.)

This is the same as what obtained in (7.24) & (7.25) by exact analysis; R in (7.25) is equal to $R_{\pi 0}$ in (7.98).

Zero-value time constant gives the result with **much less effort**. However it does not give any information on the **non-dominant** poles!

Zero-value time constant

Emitter-Follower

Now see zero-value time constant approach for emitter-follower of Fig. 7.9 where only C_π has been included. $R_{\pi 0}$ can be calculated by inserting a current source i :

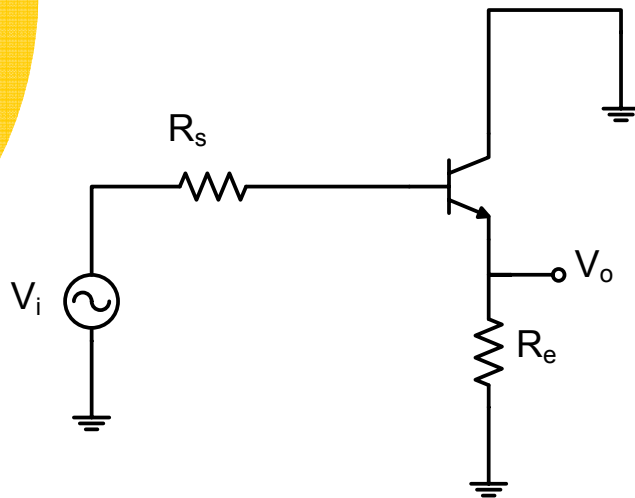


Fig. 7.9

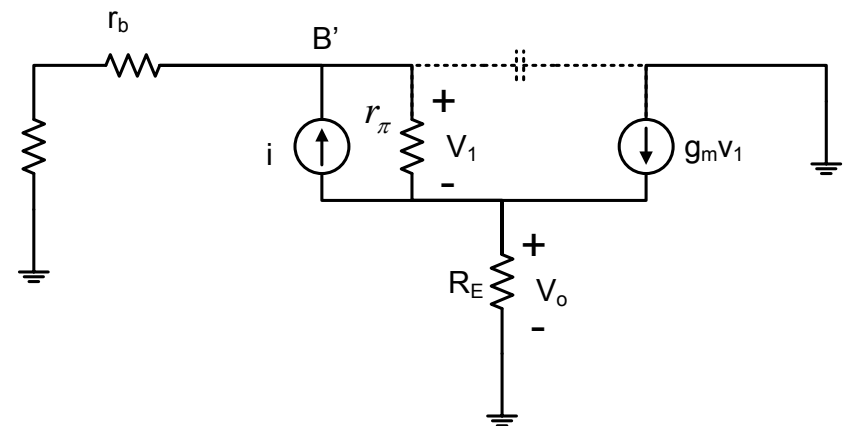


Fig. 7.17

Emitter-Follower (Cont'd)



$$\left. \begin{aligned} i &= \frac{v_1}{r_\pi} + \frac{v_1 + v_o}{R_s + r_b} & (7.99) \\ \frac{v_1}{r_\pi} - i + g_m v_1 &= \frac{v_o}{R_E} & (7.100) \end{aligned} \right\} \Rightarrow i = \frac{v_1}{r_\pi} + \frac{v_1}{R_s + r_b} + \frac{R_E}{R_s + r_b} \left(\frac{v_1}{r_\pi} + g_m v_1 - i \right)$$

$$\Rightarrow i = \frac{v_1}{r_\pi} + v_1 \frac{1 + g_m R_E}{R_s + r_b + R_E} \Rightarrow R_{\pi 0} = \frac{v_1}{i} = r_\pi \parallel \left(\frac{R_s + r_b + R_E}{1 + g_m R_E} \right) \quad (7.101)$$

Zero-Value Time-Constant Analysis

Emitter follower (Cont'd):

For C_μ we have:

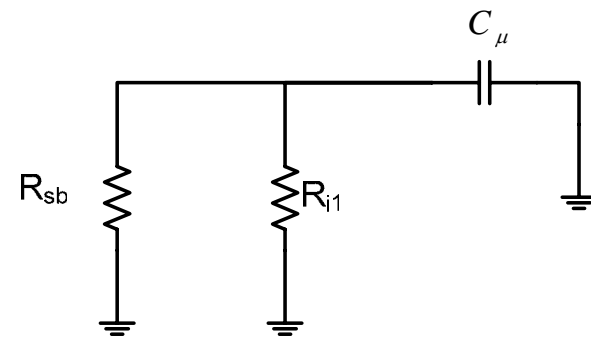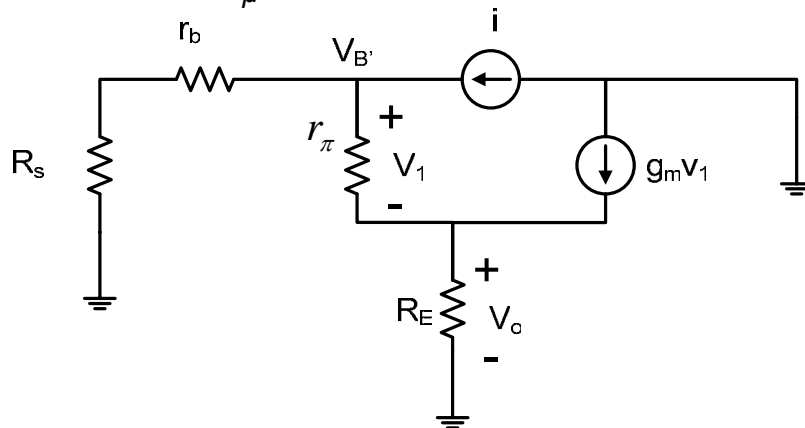

$$R_{i1} = r_\pi (1 + g_m R_E)$$

$$i = \frac{v_1 + v_o}{R_s + r_b} + \frac{v_1}{r_\pi} \Rightarrow i = v_1 \left[\frac{1}{R_s + r_b} + \frac{1}{r_\pi} + \frac{R_E}{R_s + r_b} \left(g_m + \frac{1}{r_\pi} \right) \right]$$

$$\frac{v_o}{R_E} = g_m v_1 + \frac{v_1}{r_\pi} = \left(g_m + \frac{1}{r_\pi} \right) v_1 = \frac{1 + g_m r_\pi}{r_\pi} v_1$$

$$R_{\mu 0} = \frac{v_1 + v_o}{i} = \left[(R_s + r_b) \parallel r_\pi \parallel \left(\frac{R_s + r_b}{R_E} \cdot \frac{r_\pi}{1 + g_m r_\pi} \right) \right] \left[1 + \frac{R_E}{r_\pi} (1 + g_m r_\pi) \right]$$

Zero-Value Time-Constant Analysis

for $g_m r_\pi \gg 1$

$$R_{\mu 0} = \left\{ (R_S + r_b) \parallel r_\pi \parallel \frac{R_S + r_b}{g_m R_E} \right\} (1 + g_m R_E) \\ \approx \left\{ [(R_S + r_b) \parallel r_\pi] (1 + g_m R_E) \right\} \parallel (R_S + r_b)$$

Note:

1- For a large R_S (output resistance of a preceding CE stage)

& a small resistive R_E : $(R_S + r_b) \parallel r_\pi \approx r_\pi$

$$\Rightarrow R_{\mu 0} \approx r_\pi (1 + g_m R_E) \parallel (R_S + r_b)$$

2- For a large R_S and a large R_E (like a current source), then:

$$R_{\mu 0} \approx r_\pi (1 + g_m R_E) \parallel (R_S + r_b) \approx (g_m r_\pi R_E) \parallel (R_S + r_b) \approx (R_S + r_b)$$

Note: higher R_E results in a lower $R_{\mu 0}$ (time-constant), so a higher BW!

Emitter-Follower (Cont'd)

Thus:

$$\omega_{-3\text{dB}} = \frac{1}{R_{\pi 0} C_{\pi} + R_{\mu 0} C_{\mu}} \quad (7.102)$$

Interesting to note that performing the KCL Nodal Analysis while ignoring C_{μ} results in:

$$\omega_{-3\text{dB}} = \frac{1}{R_{\pi 0} C_{\pi}} \quad (7.41)$$

Emitter-Follower (Cont'd)

Which one is the dominant pole? (7.102) is not in agreement with (7.41) obtained by KCL analysis ignoring C_μ (to be obtained by students!). Zero-value time constant tells us nothing about the dominant zero showed in the nodal analysis (ignoring C_μ):

$$z_1 = \frac{-g_m}{C_\pi} \approx -\omega_T$$

$$p_1 = -\frac{1}{C_\pi R_1} \quad \text{where} \quad R_1 = r_\pi \parallel \frac{r_b + R_E}{1 + g_m R_E}$$

Because of the dominant zero in the results obtained by the nodal analysis, the pole frequency obtained there in (7.41) can not be the -3dB frequency.

If there is a major capacitance between input and output such as C_π (in source follower) zero-value time constant can not predict ω_{-3dB} (BW) very well!

Emitter-Follower (Cont'd)

$$p_2 = - \left(\frac{1}{[(r_b + R_s) \parallel R_E] C_\mu} + \frac{1}{r_\pi C_\pi} + \frac{1}{R_E C_\pi} + \frac{g_m}{C_\pi} \right) \approx \frac{g_m}{C_\pi} \text{ for both large } R_s \text{ and } R_E$$

$C_\mu \rightarrow \infty$ (if be shorted) \Rightarrow remaining time constant is : $C_\pi (r_\pi \parallel R_E \parallel g_m)$

$C_\pi \rightarrow \infty$ (if be shorted) \Rightarrow remaining time constant is : $C_\mu [(r_b + R_s) \parallel R_E]$

There is a pole-zero cancellation! (p_2 and z_1)

Example:

Calculate poles & zero by different analyses: $C_\mu=1\text{pF}$, $C_\pi=10\text{pF}$, $R_E=2\text{k}\Omega$, $R_s=50\Omega$, $r_b=150\Omega$, $\beta=100$, $I_c=1\text{mA}$.

Solution:

1. Nodal Analysis (ignoring C_μ):

In reality, not ignoring C_μ , there are two poles such that the above p_1 is the 2nd pole

$$p_1 = 2\pi(568.2\text{MHz})$$

$$z_1 = f_T = 612\text{MHz}$$

2. Zero-Value Time Constant Analysis:

To be checked by Students!

Also No ideas about Zero or 2nd Pole

$$p_1 = \frac{1}{60\Omega(10\text{pF}) + 148\Omega(1\text{pF})} = 2\pi(212.8\text{MHz})$$

Zero-value time constant; Cascaded Common-Emitter Freq. Response

Zero-value time constant is advantageous for circuits with more than one device:

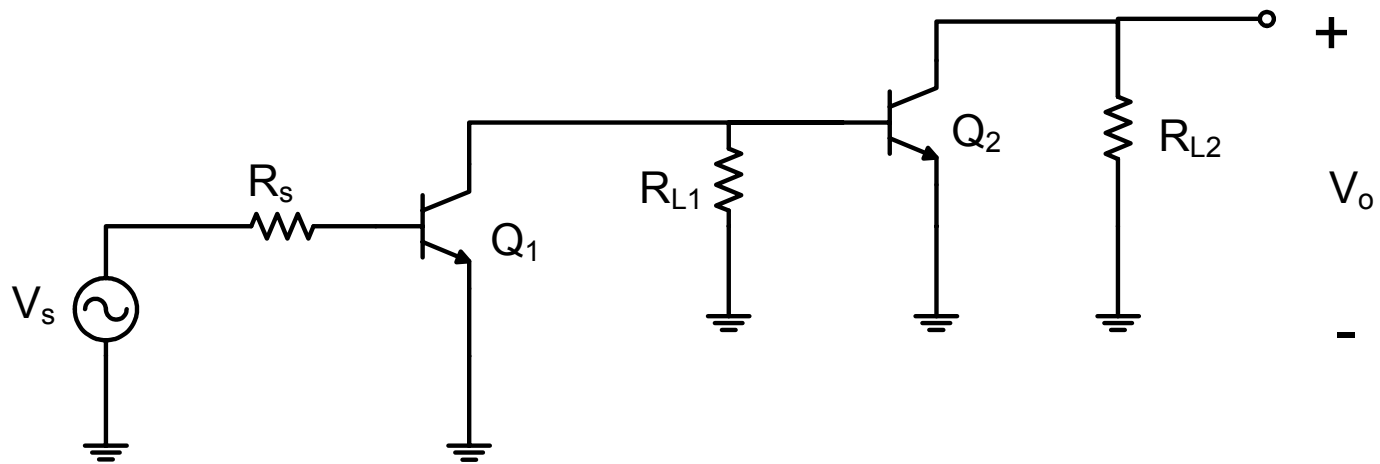


Fig.7.18: Single-ended or a differential half circuit

Example:

Cascaded Common-Emitter Freq. Response

Find ω_{-3dB} of Fig.7.18 With:

$$\begin{array}{llll} R_s = 10k \Omega & r_{b1} = r_{b2} = 400\Omega & r_{\pi1} = 20k \Omega & C_{\pi1} = 5pF \\ C_{\pi2} = 10pF & C_{\mu1} = C_{\mu2} = 1pF & R_{L1} = 10k \Omega & C_{cs1} = C_{cs2} = 2pF \\ r_{\pi2} = 10k \Omega & R_{L2} = 5k \Omega & g_{m1} = 3mA/V & g_{m2} = 6mA/V \end{array}$$

Cascaded Common-Emitter Freq. Response

Small signal:

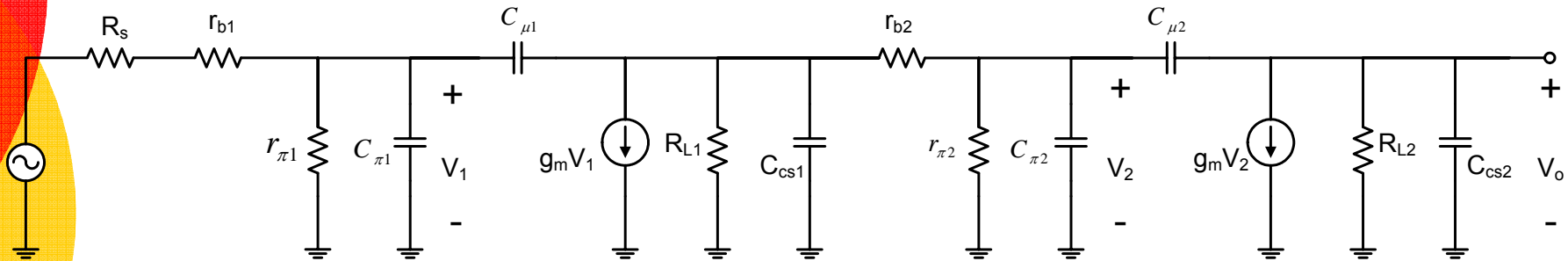


Fig. 7.19

For $C_{\mu 1}$ and $C_{\mu 2}$ Eqn. 7.96 can be applied:

$$\left\{ \begin{array}{l} C_{\mu 1} R_{\mu 01} = C_{\mu 1} R_{\pi 01} \left(1 + g_{m1} R_{L1eff} + \frac{R_{L1eff}}{R_{\pi 01}} \right) \end{array} \right. \quad (7.103)$$

$$\left\{ \begin{array}{l} C_{\mu 2} R_{\mu 02} = C_{\mu 2} R_{\pi 02} \left(1 + g_{m2} R_{L2eff} + \frac{R_{L2eff}}{R_{\pi 02}} \right) \end{array} \right. \quad (7.104)$$

Cascaded Common-Emitter Freq. Response

Where: $R_{L1eff} = R_{L1} \parallel (r_{b2} + r_{\pi2}) = 5.1k \Omega$

$$R_{L2eff} = R_{L2} = 5k \Omega$$

$$R_{\pi01} = r_{\pi1} \parallel (r_{b1} + R_{s1}) = 20k \Omega \parallel (10.4k \Omega) = 6.84k \Omega$$

$$R_{\pi01} = r_{\pi1} \parallel (r_{b1} + R_{s1}) \quad \text{where :} \quad R_{s1} = R_{L1} = 10k \Omega$$

$$R_{\pi02} = 10k \Omega \parallel (10.4k \Omega) = 5.1k \Omega$$

And for $C_{\pi1}$, $C_{\pi2}$:

$$C_{\pi1} R_{\pi01} = 5 \times 6.84ns = 34.2n \text{ sec}$$

$$C_{\pi2} R_{\pi02} = 10 \times 5.1ns = 51n \text{ sec}$$

This substituting in (7.103) and (7.104):

$$\begin{cases} C_{\mu1} R_{\mu01} = 1 \times 6.84 \left(1 + 3 \times 5.1 + \frac{5.1}{6.84} \right) ns = 116.6n \text{ sec} \\ C_{\mu2} R_{\mu02} = 1 \times 5.1 \left(1 + 6 \times 5 + \frac{5}{5.1} \right) ns = 163.2n \text{ sec} \end{cases}$$

Cascaded Common-Emitter Freq. Response

For C_{cs1} , C_{cs2} :

$$\begin{cases} C_{cs1}R_{cs01} = C_{cs1}R_{L1eff} = 2 \times 5.1n \text{ sec} = 10.2n \text{ sec} \\ C_{cs2}R_{cs02} = C_{cs2}R_{L2eff} = 2 \times 5n \text{ sec} = 10n \text{ sec} \end{cases}$$

➤ Assuming the circuit has a dominant pole, the -3dB freq. can be estimated as

$$\begin{aligned} \omega_{-3dB} &= \frac{1}{\sum T_0} = \frac{10^9}{34.2 + 51 + 116.6 + 136.2 + 10.2 + 10} \text{ rad / sec} \\ &= \frac{10^9}{385.2} \text{ rad / sec} = 2.6 \times 10^6 \text{ rad / sec} \end{aligned}$$

$$\Rightarrow f_{-3dB} = 413 \text{ kHz}$$

Cascaded Common-Emitter Freq. Response

A computer simulation gave:

$$f_{p1} = -463kHz$$

$$f_{p2} = -4.37MHz$$

$$f_{p3} = -41.06MHz$$

$$f_{p4} = -212MHz$$

$$f_{z1} = -478MHz$$

$$f_{z2} = -955MHz$$

$$\Rightarrow f_{-3dB} = -456KHz \quad \text{only 10\% error}$$